

2021_03_03_EE538_Lecture9_W2021

March 3, 2021

1 EE 538: Analog Integrated Circuit Design

1.1 Winter 2021

1.2 Instructor: Jason Silver

1.3 Python packages/modules

```
[2]: import matplotlib as mpl
from matplotlib import pyplot as plt
import numpy as np
from scipy import signal
%%matplotlib notebook

mpl.rcParams['font.size'] = 12
mpl.rcParams['legend.fontsize'] = 'large'

def plot_xy(x, y, xlabel, ylabel):
    fig, ax = plt.subplots(figsize=(10.0, 7.5));
    ax.plot(x, y, 'b');
    ax.grid();
    ax.set_xlabel(xlabel);
    ax.set_ylabel(ylabel);

def plot_xy2(x1, y1, x1label, y1label, x2, y2, x2label, y2label):
    fig, ax = plt.subplots(2, figsize = (10.0, 7.5));
    ax[0].plot(x1, y1, 'b');
    ax[0].set_ylabel(y1label)
    ax[0].grid()

    ax[1].plot(x2, y2, 'b');
    ax[1].set_xlabel(x1label)
    ax[1].set_xlabel(x2label);
    ax[1].set_ylabel(y2label);
    ax[1].grid();

    fig.align_ylabels(ax[:])
```

```

def plot_x2y(x, y1, y2, xlabel, ylabel, y1label, y2label):

    fig, ax = plt.subplots(figsize=(10.0, 7.5));
    ax.plot(x, y1, 'b')
    ax.plot(x, y2, 'r')
    ax.legend( [y1label,y2label] ,loc='upper center', ncol=5, fancybox=True,
               shadow=True, bbox_to_anchor=(0.5,1.1))
    ax.grid()
    ax.set_xlabel(xlabel)
    ax.set_ylabel(ylabel)

def plot_xy3(x, y1, y2, y3, xlabel, y1label, y2label, y3label):
    fig, ax = plt.subplots(3, figsize=(10.0,7.5))

    ax[0].plot(x, y1)
    ax[0].set_ylabel(y1label)
    ax[0].grid()

    ax[1].plot(x, y2)
    ax[1].set_ylabel(y2label)
    ax[1].grid()

    ax[2].plot(x, y3)
    ax[2].set_ylabel(y3label)
    ax[2].set_xlabel(xlabel)
    ax[2].grid()

def plot_xlogy(x, y, xlabel, ylabel):
    fig, ax = plt.subplots(figsize=(10.0, 7.5));
    ax.semilogy(x, y, 'b');
    ax.grid();
    ax.set_xlabel(xlabel);
    ax.set_ylabel(ylabel);

def plot_logxy2(x1, y1, x2, y2, x1label, y1label, x2label, y2label):
    fig, ax = plt.subplots(2, figsize = (10.0, 7.5));
    ax[0].semilogx(x1, y1, 'b');
    ax[0].set_ylabel(y1label)
    ax[0].grid()

    ax[1].semilogx(x2, y2, 'b');
    ax[1].set_xlabel(x1label)
    ax[1].set_xlabel(x2label);
    ax[1].set_ylabel(y2label);
    ax[1].grid();

    fig.align_ylabels(ax[:])

```

```

def nmos_iv_sweep(V_gs, V_ds, W, L, lmda):
    u_n = 350 # electron mobility (device parameter)
    e_ox = 3.9*8.854e-12/100; # relative permittivity
    t_ox = 9e-9*100; # oxide thickness
    C_ox = e_ox/t_ox # oxide capacitance
    V_thn = 0.7 # threshold voltage (device parameter)
    V_ov = V_gs - V_thn
    Ldn = 0.08e-6
    Leff = L - 2*Ldn

    I_d = []

    for i in range(len(V_ds)):
        I_d.append(np.piecewise(V_ds[i], [V_ds[i] < V_ov, V_ds[i] >= V_ov],
                                [u_n*C_ox*(W/Leff)*(V_gs - V_thn - V_ds[i]/
→2)*V_ds[i]*(1+lmda*V_ds[i]) ,
                                0.5*u_n*C_ox*(W/Leff)*(V_gs -
→V_thn)**2*(1+lmda*V_ds[i])]))

    return np.array(I_d)

def pmos_iv_sweep(V_sg, V_sd, W, L, lmda):
    u_p = 100 # electron mobility (device parameter)
    e_ox = 3.9*8.854e-12/100; # relative permittivity
    t_ox = 9e-9*100; # oxide thickness
    C_ox = e_ox/t_ox # oxide capacitance
    V_thp = -0.8 # threshold voltage (device parameter)
    V_ov = V_sg - np.abs(V_thp)
    Ldp = 0.09e-6
    Leff = L - 2*Ldp

    I_d = []

    for i in range(len(V_sd)):
        I_d.append(np.piecewise(V_sd[i], [V_sd[i] < V_ov, V_sd[i] >= V_ov],
                                [u_p*C_ox*(W/Leff)*(V_sg - np.abs(V_thp) - V_sd[i]/
→2)*V_sd[i]*(1+lmda*V_sd[i]) ,
                                0.5*u_p*C_ox*(W/Leff)*(V_sg - np.
→abs(V_thp))**2*(1+lmda*V_sd[i])]))

    return np.array(I_d)

def nmos_iv_sat(V_gs, V_ds, W, L, lmda):
    u_n = 350 # electron mobility (device parameter)
    e_ox = 3.9*8.854e-12/100; # relative permittivity
    t_ox = 9e-9*100; # oxide thickness

```

```

C_ox = e_ox/t_ox          # oxide capacitance
V_thn = 0.7                # threshold voltage (device parameter)
V_ov = V_gs - V_thn
Ldn = 0.08e-6
Leff = L - 2*Ldn

I_d = 0.5*u_n*C_ox*(W/Leff)*(V_gs - V_thn)**2*(1+lmda*V_ds)

return I_d

def nmos_diff_pair(V_id, I_ss, R_D, W, L, V_dd):
    u_n = 350               # electron mobility (device parameter)
    e_ox = 3.9*8.854e-12/100; # relative permittivity
    t_ox = 9e-9*100;        # oxide thickness
    C_ox = e_ox/t_ox        # oxide capacitance
    V_thn = 0.7              # threshold voltage (device parameter)
    Ldn = 0.08e-6
    Leff = L - 2*Ldn

    I_dp = I_ss/2 + 0.25*u_n*C_ox*(W/L)*V_id*np.sqrt(4*I_ss/(u_n*C_ox*(W/L)) -
→V_id**2)
    I_dm = I_ss/2 - 0.25*u_n*C_ox*(W/L)*V_id*np.sqrt(4*I_ss/(u_n*C_ox*(W/L)) -
→V_id**2)

    return I_dp, I_dm

```

2 Lecture 9 - High-gain CMOS OTA Design

2.1 Announcements

- Design Project Phase 1 posted, due Sunday March 7
 - PDF submission on Canvas
- Design Project Phase 2 posted, due Friday March 19
 - PDF submission on Canvas

2.2 Week 9


- Chapter 10 of Razavi (MOS physics)
- Chapter 9 of Razavi (frequency response)
 - Section 9.4 Common Source Stage

2.3 Overview

- Last time...
 - Feedback
 - Stability definition and criteria (Bode/root locus)
 - Damping ratio and phase margin

- Mirror poles
- Frequency response of two-stage amplifiers
- Today...
 - Miller compensation of 2-stage OTAs
 - Ahuja compensation
 - Gain-boosted structures

 2.4 Frequency response of a 2-stage amplifier



- Assuming a “large” value of C_{GD} , the two poles of the transfer function can be approximated as

$$\omega_{p1} \approx \frac{1}{R_{o1}(1 + g_{m8}R_{o2})C_{GD}} \quad (1)$$


$$\omega_{p2} \approx \frac{g_{m8}C_{GD}}{C_{GD}(C_{GS} + C_L) + C_{GS}C_L} \quad (2)$$

- The unity-gain frequency, ω_u is approximately

$$\omega_u \approx g_{m1}R_{o1}g_{m8}R_{o2} \cdot \frac{1}{g_{m8}R_{o2}R_{o1}C_{GD}} = \frac{g_{m1}}{C_{GD}} \quad (3)$$

- How do we guarantee a large enough value for C_{GD} to accomplish pole splitting?

2.5 Miller compensation

 

- We can add an explicit capacitance (e.g. an integrated “MIM” capacitor) to increase the effective value of C_{GD}
- In general, $C_c \gg C_{GD}$, such that $C_c + C_{GD} \approx C_c$
- Considering only ω_{p1} and ω_{p2} (ignoring ω_z , for the moment), the phase margin is given by

$$PM \approx 90^\circ - \tan^{-1} \frac{\omega_u}{\omega_{p2}} \quad (4)$$


$$= 90^\circ - \tan^{-1} \frac{g_{m1}(C_L + C_{GS8})}{g_{m8}C_c} \quad (5)$$

$$(6)$$

- Note that if C_L and C_c are comparable, g_{m8} should be much greater than g_{m1} to achieve a well-behaved response

```
[7]: gm1 = 1e-3
gm8 = 1e-3
ro = 100e3
R_o1 = ro/2
R_o2 = ro/2
C_GD = 10e-12
C_GS = .2e-12
C_L = 10e-12
zeta = C_GS*C_GD + C_GS*C_L+C_GD*C_L
num = [C_GD*R_o2*gm1*R_o1, -gm8*R_o2*gm1*R_o1]
den = [R_o1*R_o2*zeta, gm1*R_o1*R_o2*C_GD+R_o1*C_GS+R_o2*(C_GD+C_L), 1]
tf_CS = signal.TransferFunction(-gm1*R_o1*gm8*R_o2, den)
w, mag, phase = tf_CS.bode()
f = w/2/np.pi
```
 
```
[8]: plot_logxy2(f, mag, f, phase, 'Frequency [Hz]', 'Magnitude [dB]',
                'Frequency [Hz]', 'Phase [deg]')
```



- Even without the influence of ω_z , the phase margin is only about 45°
- What happens when we consider ω_z ?

2.6 Effect of the RHP zero on phase margin

- The expression in the numerator, $N(j\omega) = (sC_c - g_{m8})R_{o2}$ results in a zero in the right half of the complex plane

$$\omega_z = \frac{g_{m8}}{C_c} \quad (7)$$

- A zero in the right-half plane increases phase lag as well as gain magnitude, which can be detrimental to stability

$$PM \approx 90^\circ - \tan^{-1} \frac{\omega_u}{\omega_{p2}} - \tan^{-1} \frac{\omega_u}{\omega_z} \quad (8)$$

$$(9)$$


$$= 90^\circ - \tan^{-1} \frac{g_{m1}C_L}{g_{m8}C_c} - \tan^{-1} \frac{g_{m1}}{g_{m8}} \quad (10)$$

$$(11)$$

- The phase lag due to ω_z can be up to 45° (or greater) if g_{m1} and g_{m8} are comparable


```
[9]: gm1 = 1e-3
      gm8 = 1e-3
      ro = 100e3
      R_o1 = ro/2
      R_o2 = ro/2
      C_GD = 10e-12
      C_GS = .2e-12
      C_L = 10e-12
      zeta = C_GS*C_GD + C_GS*C_L+C_GD*C_L
      num = [C_GD*R_o2*gm1*R_o1, -gm8*R_o2*gm1*R_o1]
      den = [R_o1*R_o2*zeta, gm1*R_o1*R_o2*C_GD+R_o1*C_GS+R_o2*(C_GD+C_L), 1]
      tf_CS = signal.TransferFunction(num, den)
      w, mag, phase = tf_CS.bode()
      f = w/2/np.pi
```

```
[10]: plot_logxy2(f, mag, f, phase, 'Frequency [Hz]', 'Magnitude [dB]',
                  'Frequency [Hz]', 'Phase [deg]')
```

 - Here, the phase margin has decreased to zero with the inclusion of ω_z
- The effect isn't evident from the magnitude response alone, since the rolloff from ω_{p2} is countered by a 20dB/dec increase in the magnitude due to ω_z
- How do we improve the phase margin?

2.7 Moving the RHP zero

 

- We can manipulate ω_z by inserting a resistor, R_z , in series with C_c
- Properly chosen, R_z can eliminate the RHP zero altogether (pushing it to “infinite” frequency)
- This isn’t achievable in practice, since neither g_{m8} nor R_z is precisely defined (due to variations in process and temperature)
- We can instead move ω_z to the LHP, transforming phase lag into lead
- With the inclusion of R_z the expression for the zero becomes

$$\omega_z = \frac{1}{C_c(g_{m8}^{-1} - R_z)} \quad (12)$$

- Using $R_z = 1/g_{m8}$ effectively “cancels” ω_z , pushing it to infinity
- A more reliable approach is to use $R_z > 1/g_{m8}$ to move ω_z to the left-half of the complex plane
- What is a reasonable choice for the value of R_z ?

2.8 Non-dominant pole cancellation

- The modified zero location is given by


$$\omega_z = \frac{1}{C_c(g_{m8}^{-1} - R_z)} \quad (13)$$

- If we design R_z to achieve $\omega_{z,LHP} = \omega_{p1}$, this results in a value of R_z given by

$$\omega_z = \frac{1}{C_c(g_{m8}^{-1} - R_z)} = \frac{g_{m8}}{C_L + C_{GD8}} = \omega_{p1} \rightarrow \boxed{R_z = \frac{C_L + C_c + C_{GS8}}{g_{m8}C_c}} \quad (14)$$

- Moving ω_z to overlap with ω_{p2} accomplishes two things:
 1. Removes the phase lag of the RHP zero ($\omega_{z,RHP} \rightarrow \omega_{z,LHP}$)
 2. Reduces/eliminates the phase lag due to the non-dominant pole ω_{p2}

2.9 Variability in Gm2Rz

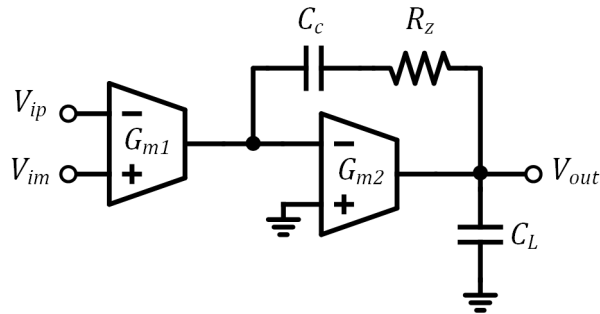

- To maximize PM we want $R_z \approx \frac{C_L + C_c}{G_{m2}C_c}$
- If $\frac{C_L + C_c}{C_c}$ is constant, we want

$$G_{m2}R_z = \frac{C_L + C_c}{C_c} = \text{constant} \quad (15)$$


- Unfortunately, G_{m2} and R_z don't track each other in terms of process and temperature variations
- However, if we could somehow define G_{m2} in terms of a resistance that varies in a similar manner to R_z , we could remove this source of uncertainty

2.10 Constant-Gm reference


- If the second stage (G_{m2}) is biased using a constant- g_m reference, variations in R_z due to process and temperature can be tracked by G_{m2}
- In this case, both R_z and R_s should be implemented on chip using the same type of resistor
- Biasing in this manner results in

$$G_{m2} = \frac{K_2}{2 \cdot R_s} \quad (16)$$

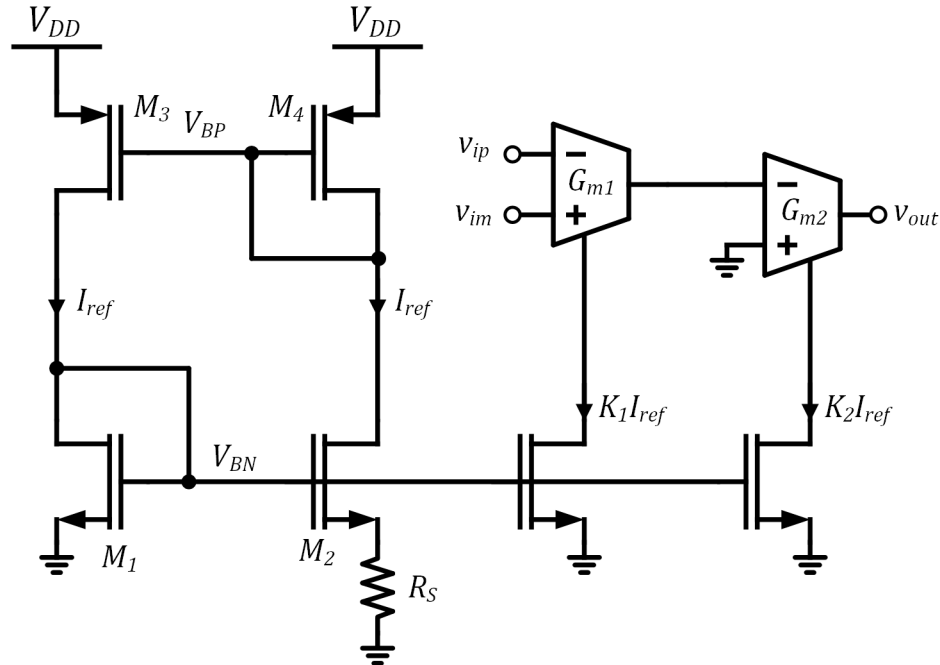- Note that g_m/I_D should be the same for M_1 of the reference and the input pair of G_{m2}



2.11 Pole-zero doublet problem

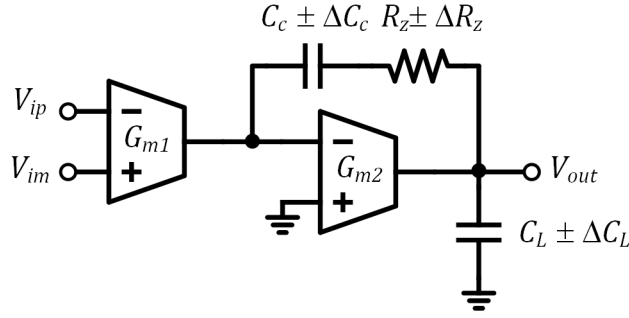


- The possibility of canceling the non-dominant pole is attractive, but in practice cancellation is imperfect
- It cannot be guaranteed that $\omega_z = \omega_{p2}$, due to variations in G_{m2} , R_z , C_c , and C_L
- Mismatch in the frequencies of ω_z and ω_{p2} results in a phenomenon known as a pole-zero “doublet,” which can significantly degrade the settling time of the OTA (particularly important for switched-capacitor applications)

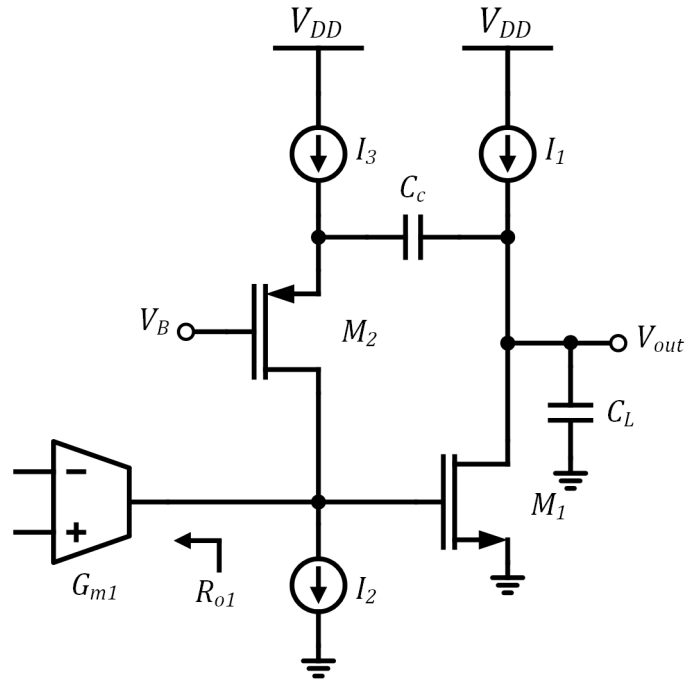
2.12 An alternate approach (Ahuja compensation)

- The feedforward path can be eliminated by the addition of a common-gate stage (M_2) in the feedback path
- The common-gate stage effectively multiplies the transconductance of M_1 by the common-gate stage gain, which is approximately $g_{m2}R_{o1}$
- The transfer function contains a zero in the *left half plane*, which can similarly be used to manipulate phase lag due to ω_{p2}
- This structure has the additional benefit of tolerance to larger values of C_L , since the non-dominant pole becomes (approximately)



$$\omega_{p2} \approx \frac{g_{m2}R_{o1}g_{m1}}{C_L} \quad (17)$$



2.13 Common-gate stage

 

  - The common-gate stage is often used as a current-input (transimpedance) amplifier, in addition to being an intrinsic structure in the cascode amplifier
- The voltage gain is the same as that of a common-source stage, but it is non-inverting



- As with other structures, R_o is determined by setting $v_i \rightarrow 0$ and finding v_t/i_t

$$R_o = \frac{v_t}{i_t} = R_L || r_o \quad (18)$$

- G_m can be found by shorting the output to ground and “measuring” the output current

$$i_{out} = -g_m v_i - \frac{v_i}{r_o} \quad (19)$$

$$G_m = \frac{i_{out}}{v_i} = -g_m - \frac{1}{r_o} \quad (20)$$

- The voltage gain of the common-gate stage is given by



$$\boxed{\frac{v_o}{v_i} = -G_m R_o \approx g_m (R_L || r_o)} \quad (21)$$

2.14 Gain boosting

- Gain-boosting can be used to enhance the effective transconductance of M_2 and M_3 and increase output impedance
- $U_{1,2}$ amplify the small-signal voltages at v_{s2} and v_{s3} to boost the small-signal transconductance currents of M_2 and M_3
- U_1 and U_2 can be implemented as single-stage OTA's with or without cascoding
- If $U_{1,2}$ are cascode amplifiers (with DC gain $\propto g_m^2 r_o^2$), the gain of the primary amplifier can be increased to

$$|A_{v0}| = G_m R_o \propto g_m^4 r_o^4 \quad (22)$$

  - Bias voltages V_{BN} and V_{BP1} should be V_{GS2}/V_{SG3} lower/higher than the target gate bias



- A_0 is the open-loop gain of the auxiliary amplifiers U_1 and U_2

- KCL for the half-circuit (plus Ohm's law for r_{o1}) gives

$$i_t = g_{m2,3}(A_0 + 1)v_s + \frac{v_t - v_s}{r_{o2,3}} = \frac{v_s}{r_{o1}} \quad (23)$$


- This results in a half-circuit impedance of

$$\frac{v_t}{i_t} = r_{o2,3} + r_{o1,4} + g_{m2,3}r_{o2,3}r_{o1,4}(A_0 + 1) \quad (24)$$

- The parallel combination of the two halves is given approximately by

$$R_o \approx [g_{m2}r_{o1}r_{o2}A_0] \parallel [g_{m3}r_{o3}r_{o4}A_0] \quad (25)$$

2.15 Implementation of U1,2

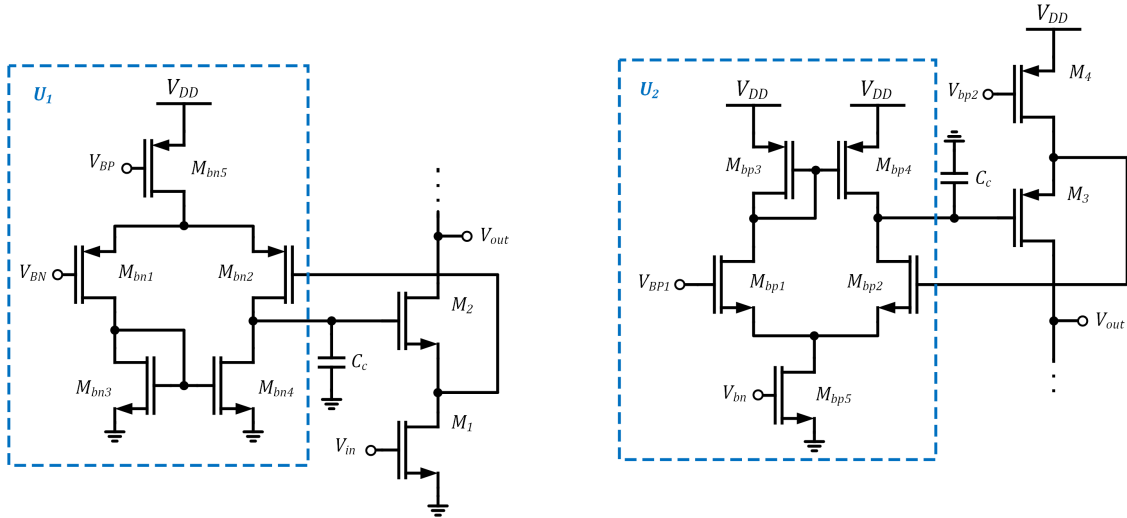

- One means of generating the regulated cascode bias is shown here
 - $U_{1,2}$ should be compensated to ensure stability of the local feedback
 - This can be accomplished by placing a compensation capacitor (C_c) between the auxiliary OTA output and small-signal ground, putting the frequency of the dominant pole at $\omega_{0,boost} \approx \frac{2}{r_o C_c}$

2.16 Summary

- 2-stage CMOS OTA's are typically compensated by increasing the Miller capacitance of the second stage to make the Miller pole dominant
- Miller compensation produces a non-dominant pole at approximately $\omega_{p2} = G_{m2}/C_L$ and a RHP zero at $\omega_z = G_{m2}/C_c$
- To alleviate the phase lag due to ω_{p2} and ω_z , ω_z can be moved to the LHP, close in frequency to ω_{p2}
- In practice, cancellation is imperfect and can result in slow setting (pole-zero doublet)

- Gain-boosting is an alternative to the 2-stage design that is simpler to compensate but adds complexity due to the required auxiliary amplifiers
- Gain-boosting results in lower output swing, so a folded cascode is often preferred