

# 2021\_01\_20\_EE538\_Lecture3\_W2021

January 23, 2021

## 1 EE 538: Analog Integrated Circuit Design

### 1.1 Winter 2021

### 1.2 Instructor: Jason Silver

### 1.3 Python packages/modules

```
[2]: import matplotlib as mpl
from matplotlib import pyplot as plt
import numpy as np
from scipy import signal
%%matplotlib notebook

mpl.rcParams['font.size'] = 12
mpl.rcParams['legend.fontsize'] = 'large'

def plot_xy(x, y, xlabel, ylabel):
    fig, ax = plt.subplots(figsize=(10.0, 7.5));
    ax.plot(x, y, 'b');
    ax.grid();
    ax.set_xlabel(xlabel);
    ax.set_ylabel(ylabel);

def plot_xy2(x1, y1, x1label, y1label, x2, y2, x2label, y2label):
    fig, ax = plt.subplots(2, figsize = (10.0, 7.5));
    ax[0].plot(x1, y1, 'b');
    ax[0].set_ylabel(y1label)
    ax[0].grid()

    ax[1].plot(x2, y2, 'b');
    ax[1].set_xlabel(x1label)
    ax[1].set_xlabel(x2label);
    ax[1].set_ylabel(y2label);
    ax[1].grid();

    fig.align_ylabels(ax[:])
```

```

def plot_xlogy(x, y, xlabel, ylabel):
    fig, ax = plt.subplots(figsize=(10.0, 7.5));
    ax.semilogy(x, y, 'b');
    ax.grid();
    ax.set_xlabel(xlabel);
    ax.set_ylabel(ylabel);

def nmos_iv_sweep(V_gs, V_ds, W, L, lmda):
    u_n = 350 # electron mobility (device parameter)
    e_ox = 3.9*8.854e-12/100; # relative permittivity
    t_ox = 9e-9*100; # oxide thickness
    C_ox = e_ox/t_ox # oxide capacitance
    V_thn = 0.7 # threshold voltage (device parameter)
    V_ov = V_gs - V_thn
    Ldn = 0.08e-6
    Leff = L - 2*Ldn

    I_d = []

    for i in range(len(V_ds)):
        I_d.append(np.piecewise(V_ds[i], [V_ds[i] < V_ov, V_ds[i] >= V_ov],
                                [u_n*C_ox*(W/Leff)*(V_gs - V_thn - V_ds[i]/
→2)*V_ds[i]*(1+lmda*V_ds[i]) ,
                                0.5*u_n*C_ox*(W/Leff)*(V_gs -
→V_thn)**2*(1+lmda*V_ds[i])]))

    return np.array(I_d)

def pmos_iv_sweep(V_sg, V_sd, W, L, lmda):
    u_p = 100 # electron mobility (device parameter)
    e_ox = 3.9*8.854e-12/100; # relative permittivity
    t_ox = 9e-9*100; # oxide thickness
    C_ox = e_ox/t_ox # oxide capacitance
    V_thp = -0.8 # threshold voltage (device parameter)
    V_ov = V_sg - np.abs(V_thp)
    Ldp = 0.09e-6
    Leff = L - 2*Ldp

    I_d = []

    for i in range(len(V_sd)):
        I_d.append(np.piecewise(V_sd[i], [V_sd[i] < V_ov, V_sd[i] >= V_ov],
                                [u_p*C_ox*(W/Leff)*(V_sg - np.abs(V_thp) - V_sd[i]/
→2)*V_sd[i]*(1+lmda*V_sd[i]) ,
                                0.5*u_p*C_ox*(W/Leff)*(V_sg - np.
→abs(V_thp))**2*(1+lmda*V_sd[i])]))

```

```

    return np.array(I_d)

def nmos_iv_sat(V_gs, V_ds, W, L, lmda):
    u_n = 350 # electron mobility (device parameter)
    e_ox = 3.9*8.854e-12/100; # relative permittivity
    t_ox = 9e-9*100; # oxide thickness
    C_ox = e_ox/t_ox # oxide capacitance
    V_thn = 0.7 # threshold voltage (device parameter)
    V_ov = V_gs - V_thn
    Ldn = 0.08e-6
    Leff = L - 2*Ldn

    I_d = 0.5*u_n*C_ox*(W/Leff)*(V_gs - V_thn)**2*(1+lmda*V_ds)

    return I_d

```

## 2 Lecture 3 - High-gain MOS Amplifier Structures

### 2.1 Announcements

- Assignment 2 posted, due Sunday January 24
  - PDF submission on Canvas


### 2.2 Week 3

- Chapter 3 of Razavi (single-stage amplifiers)
- Chapter 5 of Razavi (current mirrors)
  - Section 5.1 Basic Current Mirrors
  - Section 5.2 Cascode Current Mirrors

### 2.3 Overview

- Last time...
  - Small signal model, cont.
  - PMOS transistors
  - Common source amplifier
    - \* Passive load
    - \* Active load
  - Basic current mirrors
- Today...
  - Source degeneration
  - Cascode current mirror
  - Cascode amplifier
  - Body effect
  - Cascode biasing

## 2.4 Common-source amplifier (review)

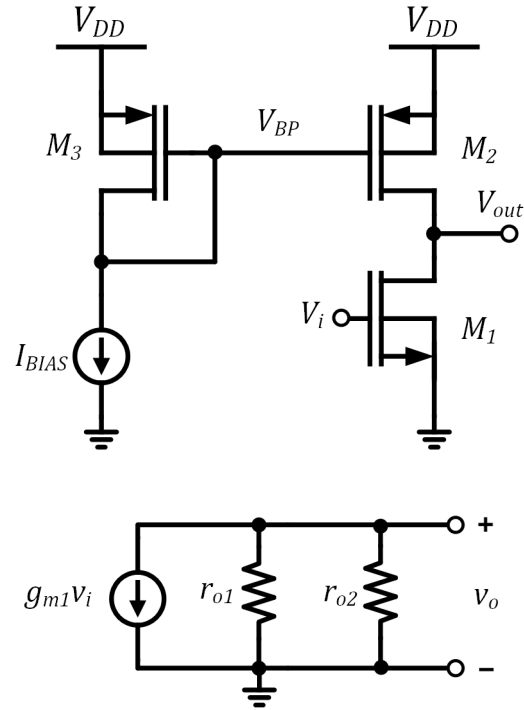


$$\frac{v_o}{v_i} = -G_m \cdot R_o = g_{m1} \cdot r_{o1} \frac{\frac{1}{\lambda_p I_{D2}}}{\frac{1}{\lambda_n I_{D2}} + \frac{1}{\lambda_p I_{D2}}} \quad (1)$$

$$(2)$$

$$= \frac{1}{\lambda_n \cdot V_{OV1}} \frac{\lambda_n}{\lambda_p + \lambda_n} = \boxed{\frac{g_{m1} r_{o1}}{3}} \quad (3)$$

- Compared to the passively-loaded stage, higher gain is achieved by increasing output resistance using an active load  $r_{o2}$
- Bias voltage  $V_{BP}$  is produced using the current mirror formed by  $M_2, M_3$

## 2.5 Current mirror sizing

 

$$V_{SG2} = V_{SG1} \quad (4)$$


$$I_{BIAS} = I_{D1} = \frac{1}{2} \mu_p C_{ox} \left( \frac{W}{L} \right)_1 (V_{SG1} - |V_{thp}|)^2 \quad (5)$$

$$I_{D2} = \frac{1}{2} \mu_p C_{ox} \left( \frac{W}{L} \right)_2 (V_{SG2} - |V_{thp}|)^2 \quad (6)$$

$$\frac{(W/L)_2}{(W/L)_1} = K \rightarrow \boxed{I_{D2} = K \cdot I_{BIAS}} \quad (7)$$

- When sizing current mirrors, we assume infinite output impedance (i.e.  $\lambda = 0$ ) since  $V_o$  isn't constant
- We then select an integer ratio of  $(W/L)_2$  to  $(W/L)_1$  to achieve a specific output current

## 2.6 Current source output resistance

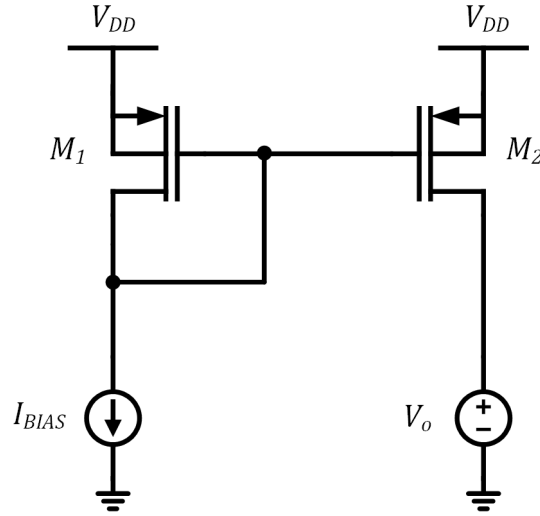

$$\frac{1}{R_o} = \frac{\partial I_{D2}}{\partial V_o} \quad (8)$$

$$(9)$$

$$= \frac{\partial}{\partial V_o} \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG2} - |V_{thp}|)^2 [1 + \lambda_p (V_{DD} - V_o)] \quad (10)$$


$$(11)$$

$$\approx \lambda_p I_{D2} \quad (12)$$

$$\rightarrow R_o \approx \frac{1}{\lambda_p I_{D2}} = r_{o2} \quad (13)$$


- The output resistance of a current source determines its sensitivity to output voltage
- In the case of a current source based on a single *MOSFET*, the output resistance is equal to the intrinsic output resistance of the transistor,  $r_o$
- Assume that we design our circuit for a nominal operating point of  $V_o = 1.5V$  and  $I_{D2} = 100\mu A$
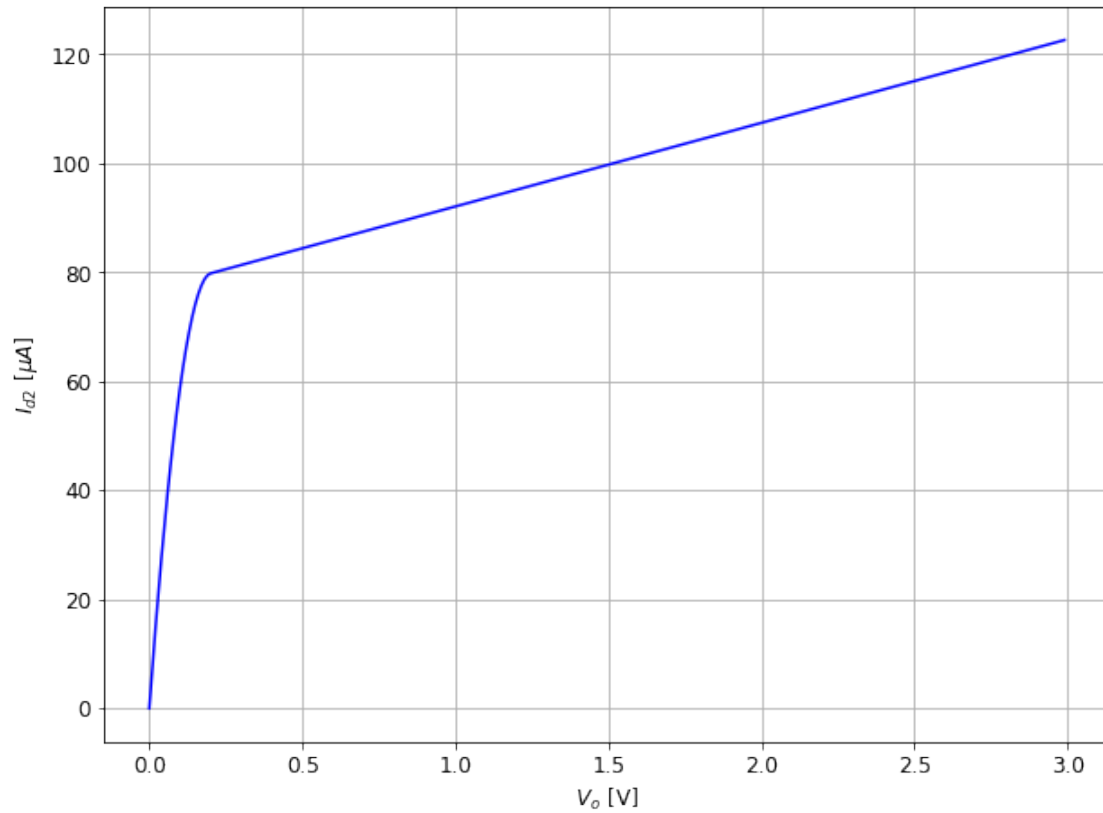
```
[16]: lambda_p = 0.2
V_o = np.arange(0, 3, 0.01)
I_d2 = pmos_iv_sweep(1, V_o, 100, 1, lambda_p)
plot_xy(V_o, 1e6*I_d2, r'$V_{o}$ [V]', r'$I_{d2}$ [$\mu A$]')
```



- The finite output resistance of  $M_2$  causes  $I_{out}$  to vary significantly with  $V_o$  ( $\pm 20\%$ !)
- This will affect various circuit parameters, such as  $g_m$ , bandwidth, stability, etc.
- How do we reduce the variability in  $I_{d2}$ ?


## 2.7 Source degeneration

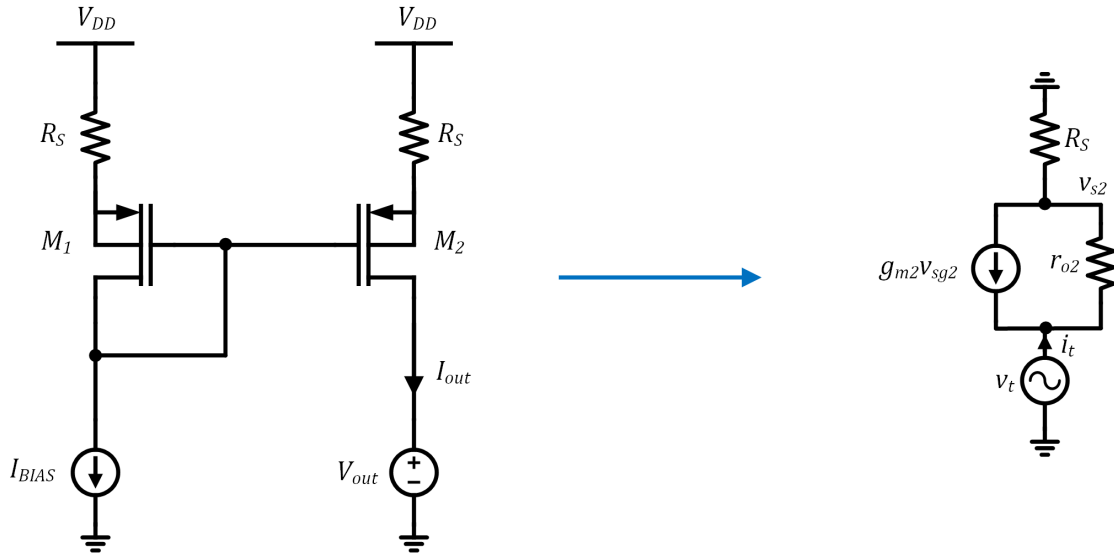

$$R_o = \frac{v_t}{i_t} = ? \quad (14)$$

- Resistor between source of PMOS and  $V_{DD}$  is referred to as “source degeneration”
- This is a form of negative feedback that increases the output resistance of the current source over that of a MOS transistor alone

## 2.8 Small-signal behavior

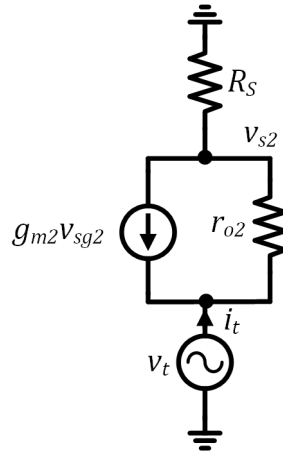

$$i_t = \frac{v_{s2}}{R_S} = -g_{m2}v_{sg2} + \frac{v_t - v_{s2}}{r_{o2}} \quad (15)$$

$$v_{s2} = i_t R_S \quad (16)$$

$$R_o = \frac{v_t}{i_t} = r_{o2}(1 + g_{m2}R_S) + R_S \quad (17)$$



- As  $v_t$  increases, so does the source voltage  $v_{s2}$
- This results in an increase in the current  $g_{m2}v_{s2}$ , which is in the direction opposite to  $i_t$
- The resulting negative feedback increases the output resistance of the degenerated current source

## 2.9 Increased output resistance

- If we assume a voltage drop across  $R_S$  of  $200mV$ , then

$$R_S = \frac{0.2V}{I_{D2}} \quad (18)$$

- The output resistance of the degenerated current source is


$$R_o = r_{o2}(1 + g_{m2}R_S) + R_S = r_{o2} \left( 1 + \frac{2I_{D2}}{V_{OV2}} \frac{0.2V}{I_{D2}} \right) + R_S \quad (19)$$

- For  $V_{OV2} = 0.2V$ , we obtain

$$R_o = 3r_{o2} + R_S \approx 3r_{o2} \quad (20)$$

- The original output resistance,  $r_{o2}$ , is increased by the gain of the feedback loop,  $g_{m2}R_S$ , and added to the series resistance  $R_S$
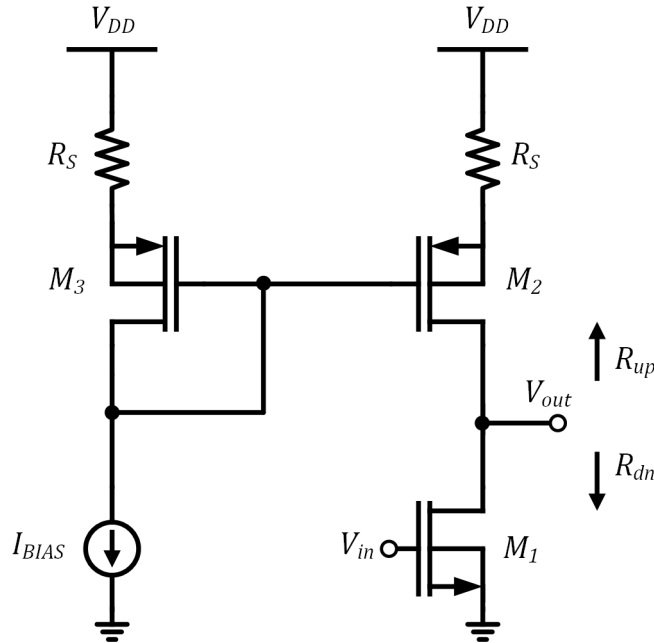
## 2.10 Common-source amplifier with degeneration



$$R_{up} = r_{o2}(1 + g_{m2}R_S) + R_S \quad (21)$$

$$R_{dn} = r_{o1} \quad (22)$$

$$R_o = R_{up} || R_{dn} \quad (23)$$

$$(24)$$

$$= [r_{o2}(1 + g_{m2}R_S) + R_S] || r_{o1} \quad (25)$$

$$(26)$$

$$\boxed{A_v = -g_{m1}R_o} \quad (27)$$

- The amplifier output resistance is the parallel combination of the current source resistance and  $r_{o1}$
- Let's take a look at a typical value for this...
- Recall that for  $R_S = 0.2V/I_{D2}$  and  $V_{OV2} = 0.2V$ , the output resistance of the degenerated current source is

$$R_{up} = 3r_{o2} + R_S \approx 3r_{o2} \quad (28)$$

- This small-signal resistance appears in parallel with  $R_{dn} = r_{o1}$ , resulting in

$$R_o \approx 3r_{o2} || r_{o1} \quad (29)$$

- Using our process model parameters  $\lambda_p = 0.2V^{-1}$  and  $\lambda_n = 0.1V^{-1}$ , we find

$$R_o \approx 3r_{o2} || r_{o1} = \frac{(\frac{3}{\lambda_p I_{D2}})(\frac{1}{\lambda_n I_{D2}})}{\frac{3}{\lambda_p I_{D2}} + \frac{1}{\lambda_n I_{D2}}} = \frac{(\frac{3}{\lambda_p I_{D2}})(\frac{1}{\lambda_n I_{D2}})}{\frac{3\lambda_n + \lambda_p}{\lambda_n \lambda_p I_{D2}}} = \frac{3}{(3\lambda_n + 2\lambda_n)I_{D2}} = \frac{3}{5}r_{on} \quad (30)$$

- We have increased the output resistance (and hence the gain) of the common-source amplifier by about 20%
- Can we do better?
- What if  $R_S = r_{op}$ ?
- In this case, the output resistance of the current source becomes


$$R_{up} = r_{op}(1 + g_{m2}r_{op}) + r_{op} \quad (31)$$

- $g_{m2}r_{op}$  is equal to the intrinsic gain of a PMOS transistor. If we take this to be at least  $10V/V$ , the current source output impedance becomes

$$R_{up} = r_{op}(1 + g_{m2}r_{op}) + r_{op} \geq 12r_{op} \quad (32)$$

- This is more than an order of magnitude higher than the output impedance of a single transistor. How do we achieve this?
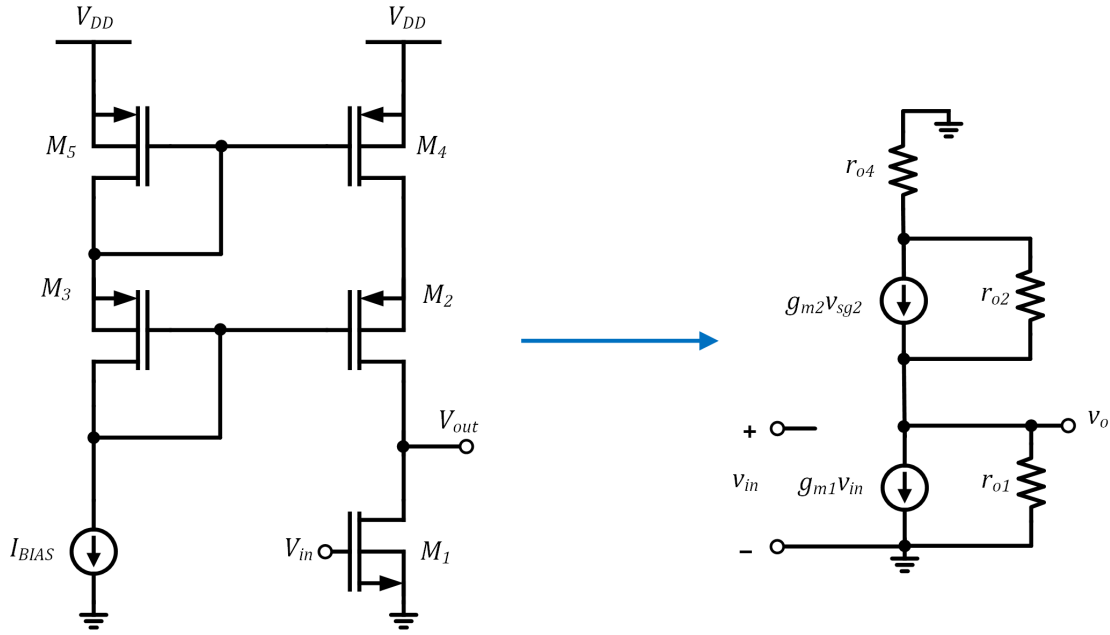
## 2.11 Common-source amplifier with cascode load



- “Cascodeing” is source degeneration using  $r_o$  in place of  $R_S$
- The DC gain of this configuration is

$$A_v = -G_m \cdot R_o = -g_{m1} \cdot r_{o1} || [r_{o2}(1 + g_{m2}r_{o4}) + r_{o4}] \approx -g_{m1}r_{o1} \quad (33)$$

- By setting the output impedance of the current source to be much greater than that of  $M_1$ , our gain is nearly equal to the intrinsic gain of  $M_1$

## 2.12 Summary (so far)

- Common-source amplifier with resistive load provides only modest gain

$$|A_v| \approx g_{m1}R_D = \frac{2I_{D1}}{V_{OV1}} \frac{V_{DD}/2}{I_{D1}} = \frac{V_{DD}}{V_{OV1}} \quad (34)$$

- An active load increases this slightly

$$|A_v| = g_{m1} \cdot r_{o1} || r_{o2} \approx g_{m1} \frac{r_{o1}}{3} \quad (35)$$


- Source degeneration increases output resistance of current source and (slightly) increases gain

$$|A_v| = g_{m1} \cdot r_{o1} || [r_{o2}(1 + g_{m2}R_S) + R_S] \approx \frac{3}{5} g_{m1}r_{o1} \quad (36)$$

- The cascode current source significantly increases output resistance of the current source/active load


$$|A_v| = g_{m1} \cdot r_{o1} || [r_{o2}(1 + g_{m2}r_{o4}) + r_{o4}] \approx g_{m1}r_{o1} \quad (37)$$

### 2.13 Common-source with cascode load

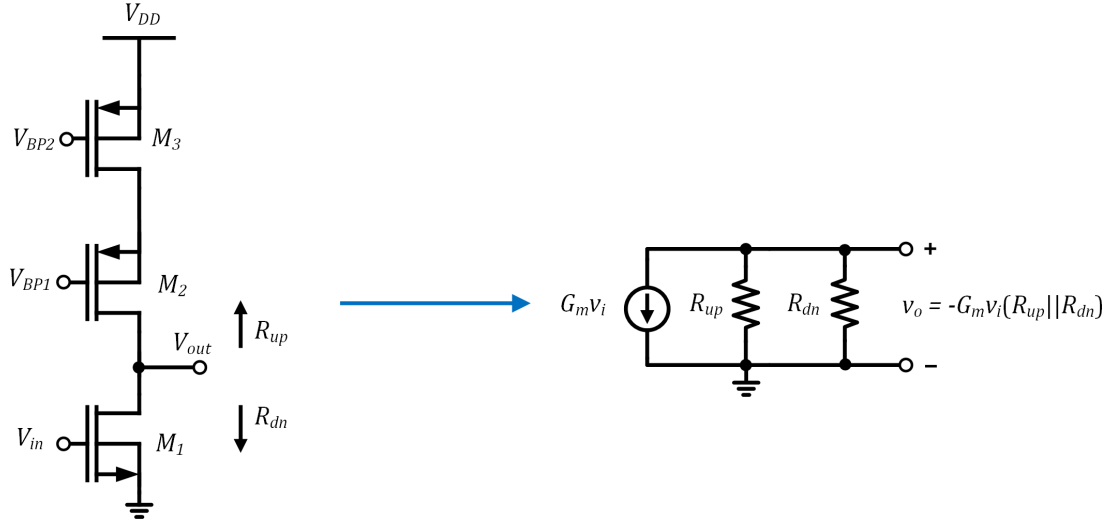

- $R_{up} \approx g_{m2}r_{o2}r_{o3}$ , while  $R_{dn} = r_{o1}$
- Cascode current-source load impedance ( $R_{up}$ ) is  $\sim g_m r_o$  times higher than  $r_{o1}$  ( $R_{dn}$ )
- If we can increase  $R_{dn}$  by the same factor, we can significantly increase our gain
- How do we accomplish this?

## 2.14 Cascode amplifier

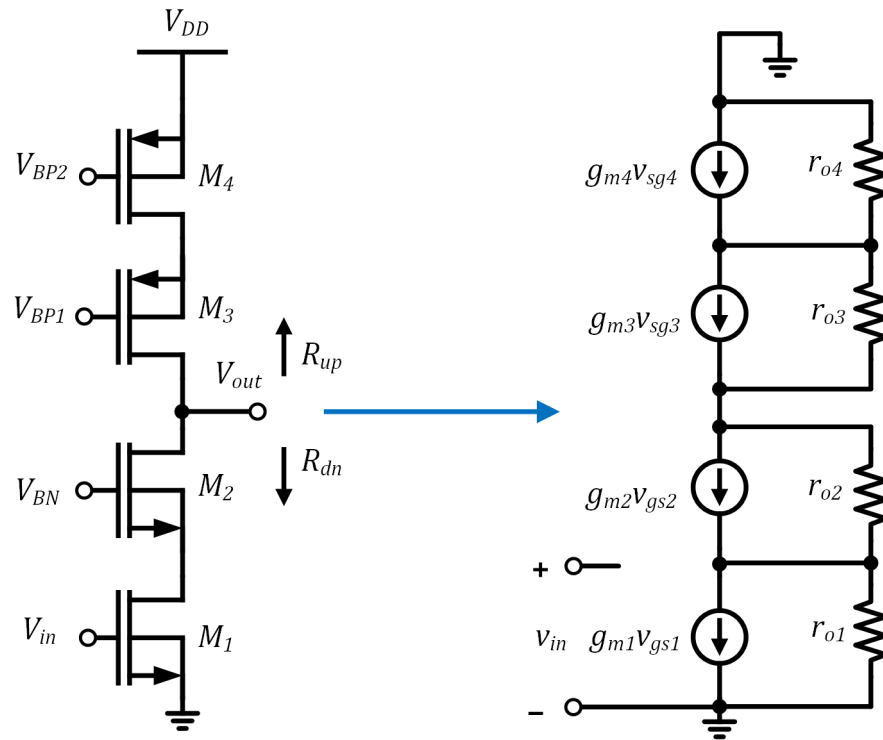


- A “fully cascoded” amplifier consists of symmetric stacks of NMOS and PMOS devices
- Recall that  $R_{up}$  is given by

$$R_{up} = r_{o3}(1 + g_{m3}r_{o4}) + r_{o4} \approx g_{m3}r_{o3}r_{o4} \quad (38)$$

- What about  $R_{dn}$ ?
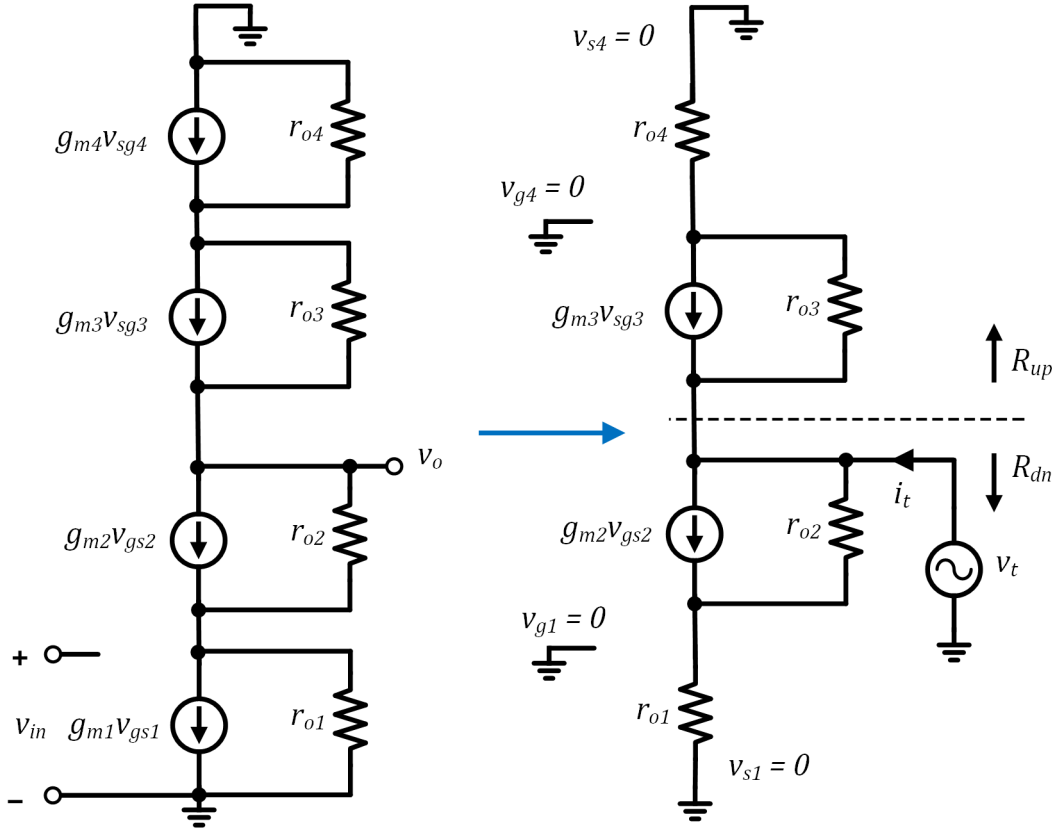
## 2.15 Cascode amplifier output impedance ( $R_o$ )




- Input voltage ( $v_{g1}$ ) is set to zero when determining  $R_o$  (Thevenin approach)
- Based on the symmetry of  $R_{up}$ ,  $R_{dn}$ , we can directly write

$$R_{dn} = r_{o2}(1 + g_{m2}r_{o1}) + r_{o1} \approx g_{m2}r_{o2}r_{o1} \quad (39)$$

- The output impedance is the parallel combination of the two:

$$R_o \approx g_{m2}r_{o2}r_{o1} || g_{m3}r_{o3}r_{o4} \approx \frac{g_m r_o^2}{2} \quad (40)$$
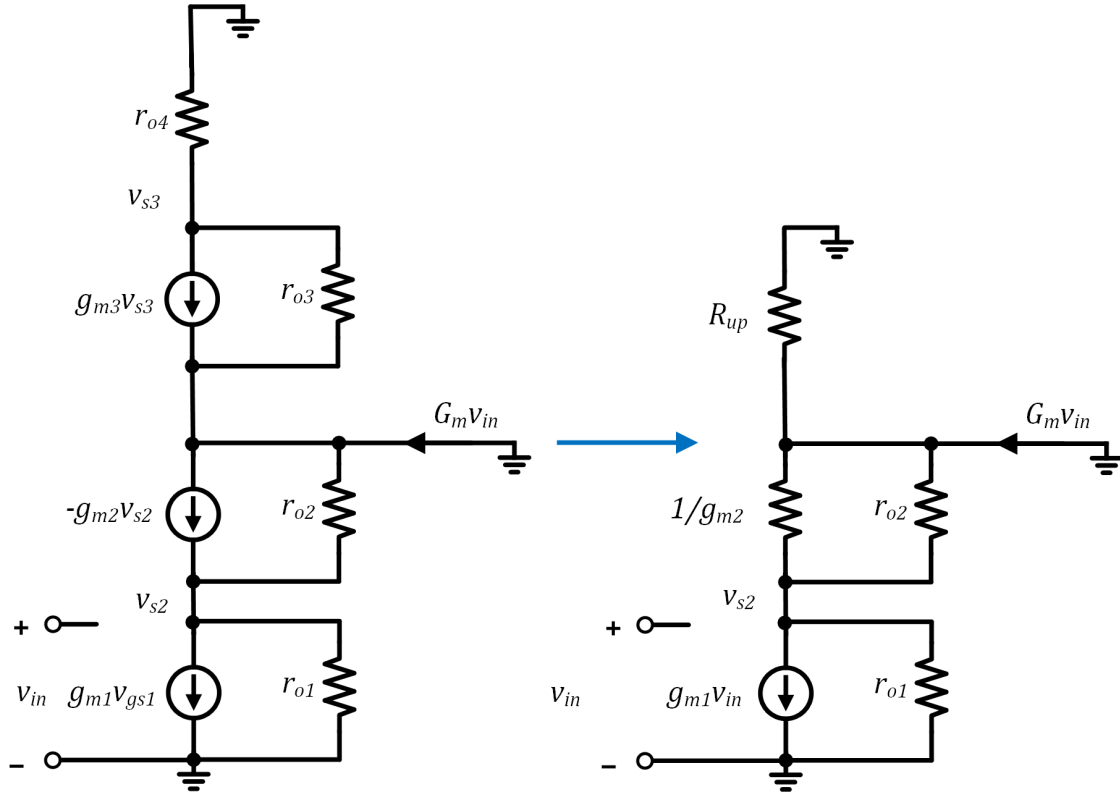
## 2.16 Cascode amplifier output impedance ( $G_m$ )




- Current through  $r_{o1}$  shunted by parallel combination of  $1/g_{m2}$  and  $r_{o2}$ :

$$G_mv_{in} = g_{m1}v_{in} \cdot \frac{r_{o1}}{\frac{1}{g_{m2}} || r_{o2} + r_{o1}} \approx g_{m1}v_{in} \quad (41)$$

- As long as  $r_{o1}, r_{o2} \gg 1/g_{m1}$ ,  $G_m$  is approximately equal to  $g_{m1}$

## 2.17 Cascode amplifier voltage gain

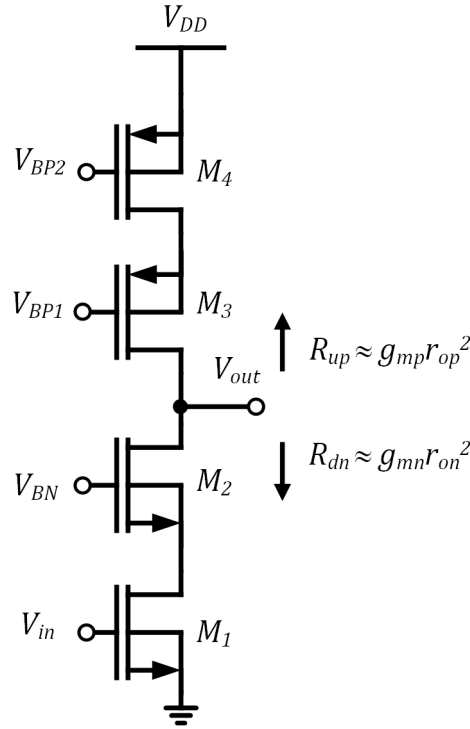

$$A_v = \frac{v_{out}}{v_{in}} \quad (42)$$

$$(43)$$

$$= -G_m \cdot R_o \quad (44)$$

$$(45)$$

$$\approx \boxed{-g_{m1}[g_{m3}r_{op}^2 || g_{m2}r_{on}^2]} \quad (46)$$


- $R_{up}$  and  $R_{dn}$  both based on  $r_o$  and scaled by  $g_m r_o$  (degeneration)
- Gain is approximately  $g_m r_o$  times higher than that of a common source with active load
- Let's put some numbers to this...
- In our Level 1 model,  $\lambda_n = 0.1V^{-1}$
- To achieve high gain, we want to use a relatively low overdrive voltage, say  $200mV$
- For simplicity, let's assume  $g_{mn}r_{on} = g_{mp}r_{op} = g_m r_o$ . The cascode amplifier gain is thus

$$|A_v| \approx \frac{g_m^2 r_o^2}{2} = \left( \frac{I_D}{V_{OV}} \frac{1}{\lambda I_D} \right)^2 = 2,500V/V \quad (47)$$

- By "cascodeing," we increase our gain from  $30dB$  with a resistive load to nearly  $70dB$ !
- Our actual gain will typically be a bit lower than this, since  $g_m$  and  $r_o$  won't be the same for all devices




## 2.18 Cascode bulk connections

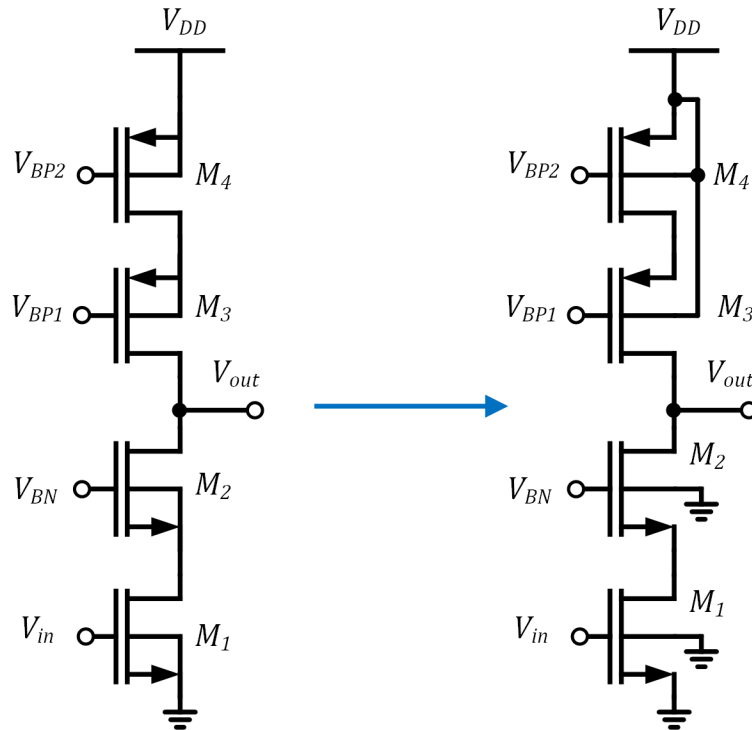


- In the cascode and source-degenerated structures, *PMOS/NMOS* source terminals may not be connected to  $V_{DD}/GND$
- Whereas *PMOS* devices are fabricated in *n-wells* and can have independent source potentials, *NMOS* bulks comprise the chip substrate and must be biased at the same potential (0V, in most cases)
- Both the large- and small-signal behavior of the *MOSFET* are affected by nonzero values of  $V_{bs}$  via modulation of the threshold voltage

## 2.19 Definition of threshold voltage

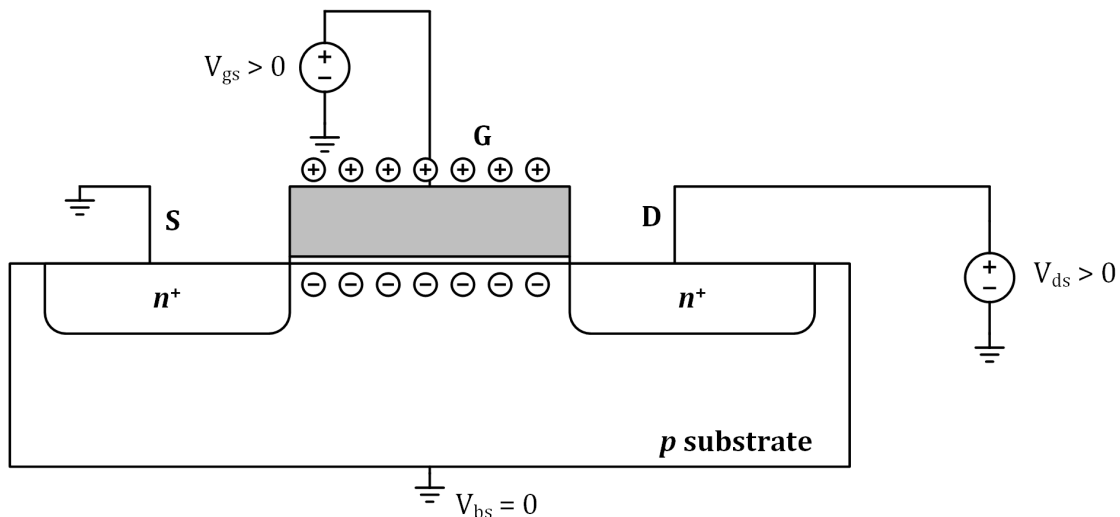

- As  $V_{gs}$  increases from 0, holes are repelled from the substrate region under the gate, leaving behind a negatively-charged depletion region
- Charge balance requires that positive gate charge mirror the immobile depletion charge
- As  $V_{gs}$  continues to increase, electrons are attracted from source and drain to form an inversion layer


## 2.20 Body effect ( $V_{bs} < 0$ )

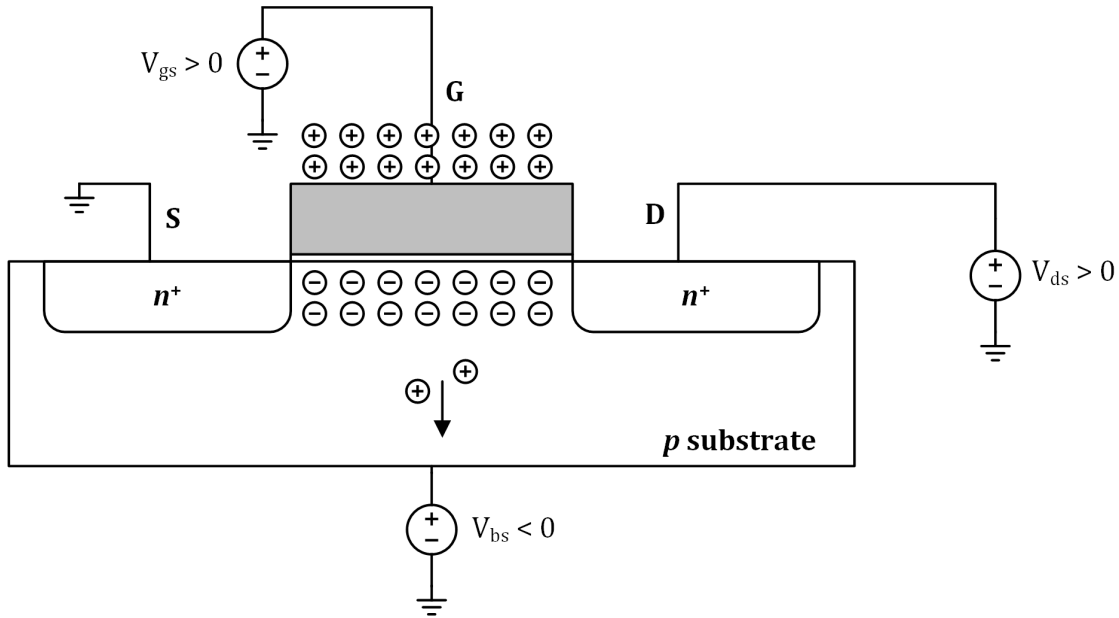

- For  $V_{bs} < 0$ , some holes are pulled from the interface toward the bulk terminal, resulting in more negative charge in the depletion region
- More positive gate charge is thus required to form an inversion layer, increasing  $V_{th}$
- The threshold voltage thus increases with increasing  $V_{sb}$ , and is defined as

$$V_{th} = V_{th0} + \gamma(\sqrt{2\phi_F + V_{sb}} - \sqrt{2\phi_F}) \quad (48)$$


## 2.21 Body effect (small signal)

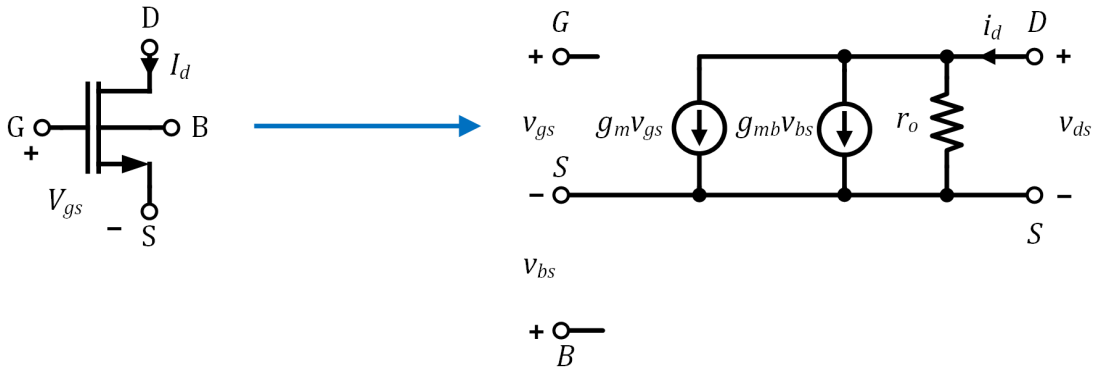

$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}} = g_m \frac{\gamma}{2\sqrt{2\phi_F + V_{SB}}} = \eta g_m \quad (49)$$


- When  $v_{bs} \neq 0$ , the bulk terminal acts as a second “gate” (body effect is often referred to as the “back-gate” effect)
- A typical range for  $\gamma$  is between 0.1 and 0.5, depending on the process technology
- Affects source-degenerated, cascode, source follower, and common-gate configurations
- Only needs to be considered when  $v_{bs} \neq 0$

## 2.22 Cascode biasing

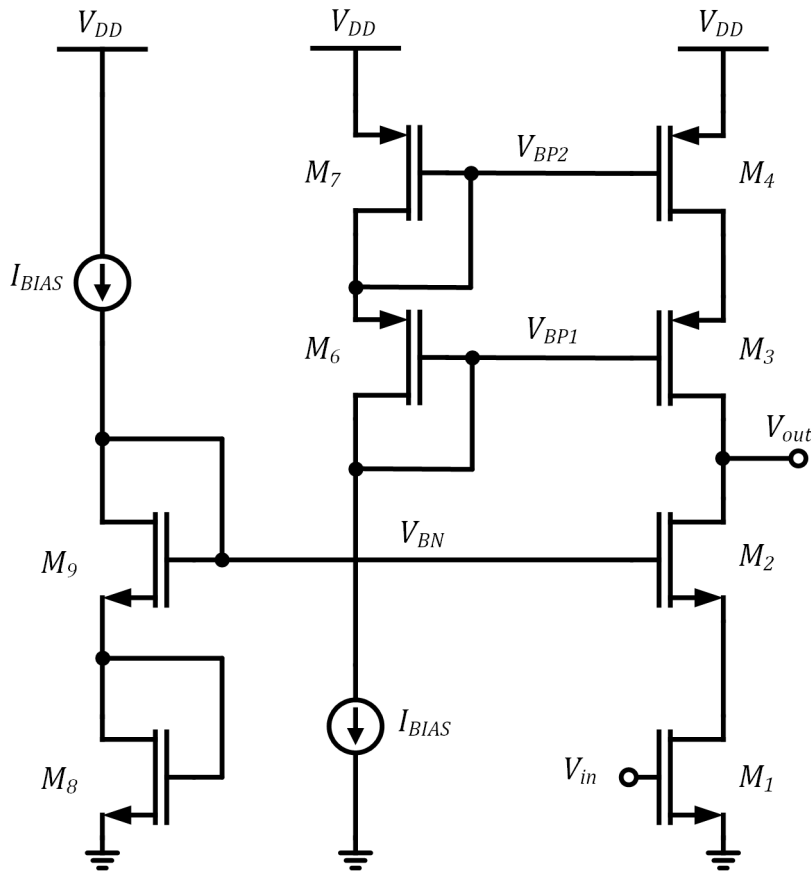

- Here is one possible bias configuration (of several) for a cascode amplifier
- A cascode current mirror ( $M_{3,4}, M_{6,7}$ ) is used to set the bias voltages  $V_{BP1}$  and  $V_{BP2}$
- $V_{BN}$  establishes a gate voltage for  $M_2$ , while a diode-connected  $M_8$  ensures that  $M_2$ 's source is at a high enough potential to keep  $M_1$  in saturation

## 2.23 Cascode voltage swing

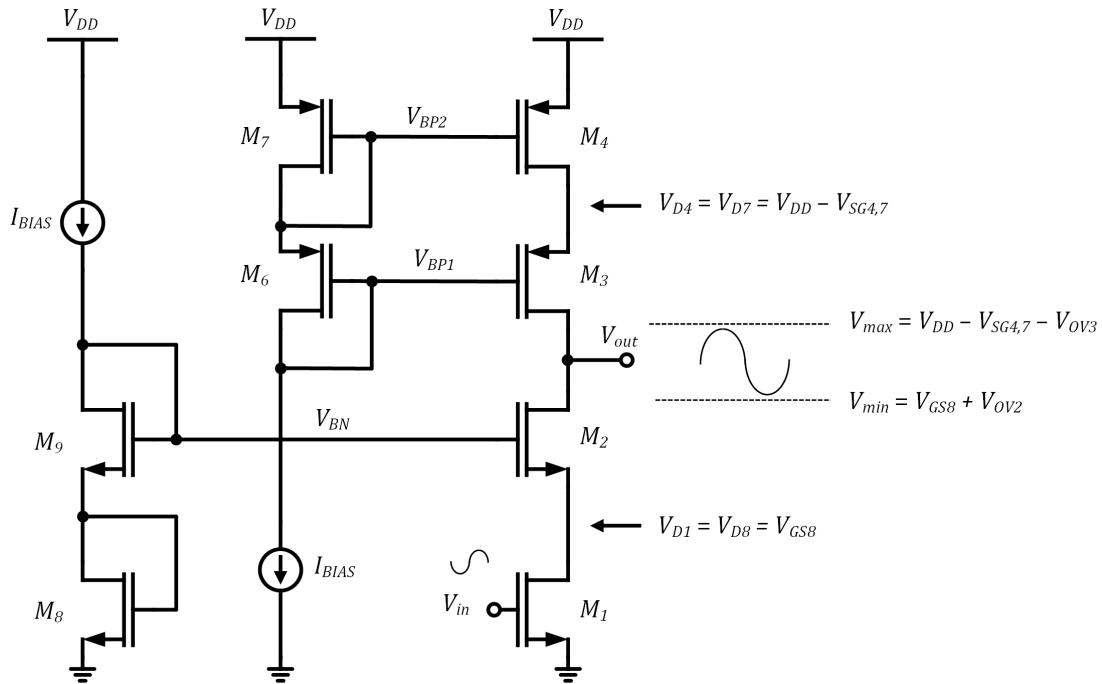

## 2.24 Summary

- Degeneration and cascoding use negative feedback to significantly increase the output resistance of the simple current source
- Higher output resistance means greater precision in current mirrors, and higher gain in amplifiers
- Adding a cascode transistor also increases the output resistance of the input path
- The gain of the cascode amplifier is approximately  $g_m r_o$  times higher than that of a common-source amplifier with active load
- Device stacking also results in the body effect, which should be considered during design
- The increased output resistance comes at the cost of lower output swing, due to stacking of more transistors