

# 2021\_02\_17\_EE538\_Lecture7\_W2021

February 16, 2021

## 1 EE 538: Analog Integrated Circuit Design

### 1.1 Winter 2021

### 1.2 Instructor: Jason Silver

### 1.3 Python packages/modules

```
[73]: import matplotlib as mpl
from matplotlib import pyplot as plt
import numpy as np
from scipy import signal
%%matplotlib notebook

mpl.rcParams['font.size'] = 12
mpl.rcParams['legend.fontsize'] = 'large'

def plot_xy(x, y, xlabel, ylabel):
    fig, ax = plt.subplots(figsize=(10.0, 7.5));
    ax.plot(x, y, 'b');
    ax.grid();
    ax.set_xlabel(xlabel);
    ax.set_ylabel(ylabel);

def plot_xy2(x1, y1, x1label, y1label, x2, y2, x2label, y2label):
    fig, ax = plt.subplots(2, figsize = (10.0, 7.5));
    ax[0].plot(x1, y1, 'b');
    ax[0].set_ylabel(y1label)
    ax[0].grid()

    ax[1].plot(x2, y2, 'b');
    ax[1].set_xlabel(x1label)
    ax[1].set_xlabel(x2label);
    ax[1].set_ylabel(y2label);
    ax[1].grid();

    fig.align_ylabels(ax[:])
```

```

def plot_x2y(x, y1, y2, xlabel, ylabel, y1label, y2label):

    fig, ax = plt.subplots(figsize=(10.0, 7.5));
    ax.plot(x, y1, 'b')
    ax.plot(x, y2, 'r')
    ax.legend( [y1label,y2label] ,loc='upper center', ncol=5, fancybox=True,
               shadow=True, bbox_to_anchor=(0.5,1.1))
    ax.grid()
    ax.set_xlabel(xlabel)
    ax.set_ylabel(ylabel)

def plot_xy3(x, y1, y2, y3, xlabel, y1label, y2label, y3label):
    fig, ax = plt.subplots(3, figsize=(10.0,7.5))

    ax[0].plot(x, y1)
    ax[0].set_ylabel(y1label)
    ax[0].grid()

    ax[1].plot(x, y2)
    ax[1].set_ylabel(y2label)
    ax[1].grid()

    ax[2].plot(x, y3)
    ax[2].set_ylabel(y3label)
    ax[2].set_xlabel(xlabel)
    ax[2].grid()

def plot_xlogy(x, y, xlabel, ylabel):
    fig, ax = plt.subplots(figsize=(10.0, 7.5));
    ax.semilogy(x, y, 'b');
    ax.grid();
    ax.set_xlabel(xlabel);
    ax.set_ylabel(ylabel);

def nmos_iv_sweep(V_gs, V_ds, W, L, lmda):
    u_n = 350 # electron mobility (device parameter)
    e_ox = 3.9*8.854e-12/100; # relative permittivity
    t_ox = 9e-9*100; # oxide thickness
    C_ox = e_ox/t_ox # oxide capacitance
    V_thn = 0.7 # threshold voltage (device parameter)
    V_ov = V_gs - V_thn
    Ldn = 0.08e-6
    Leff = L - 2*Ldn

    I_d = []

    for i in range(len(V_ds)):

```

```

        I_d.append(np.piecewise(V_ds[i], [V_ds[i] < V_ov, V_ds[i] >= V_ov],
                                [u_n*C_ox*(W/Leff)*(V_gs - V_thn - V_ds[i]/
→2)*V_ds[i]*(1+lmda*V_ds[i]) ,
                                0.5*u_n*C_ox*(W/Leff)*(V_gs -
→V_thn)**2*(1+lmda*V_ds[i]))))

    return np.array(I_d)

def pmos_iv_sweep(V_sg, V_sd, W, L, lmda):
    u_p = 100 # electron mobility (device parameter)
    e_ox = 3.9*8.854e-12/100; # relative permittivity
    t_ox = 9e-9*100; # oxide thickness
    C_ox = e_ox/t_ox # oxide capacitance
    V_thp = -0.8 # threshold voltage (device parameter)
    V_ov = V_sg - np.abs(V_thp)
    Ldp = 0.09e-6
    Leff = L - 2*Ldp

    I_d = []

    for i in range(len(V_sd)):
        I_d.append(np.piecewise(V_sd[i], [V_sd[i] < V_ov, V_sd[i] >= V_ov],
                                [u_p*C_ox*(W/Leff)*(V_sg - np.abs(V_thp) - V_sd[i]/
→2)*V_sd[i]*(1+lmda*V_sd[i]) ,
                                0.5*u_p*C_ox*(W/Leff)*(V_sg - np.
→abs(V_thp))**2*(1+lmda*V_sd[i]))))

    return np.array(I_d)

def nmos_iv_sat(V_gs, V_ds, W, L, lmda):
    u_n = 350 # electron mobility (device parameter)
    e_ox = 3.9*8.854e-12/100; # relative permittivity
    t_ox = 9e-9*100; # oxide thickness
    C_ox = e_ox/t_ox # oxide capacitance
    V_thn = 0.7 # threshold voltage (device parameter)
    V_ov = V_gs - V_thn
    Ldn = 0.08e-6
    Leff = L - 2*Ldn

    I_d = 0.5*u_n*C_ox*(W/Leff)*(V_gs - V_thn)**2*(1+lmda*V_ds)

    return I_d

def nmos_diff_pair(V_id, I_ss, R_D, W, L, V_dd):
    u_n = 350 # electron mobility (device parameter)
    e_ox = 3.9*8.854e-12/100; # relative permittivity
    t_ox = 9e-9*100; # oxide thickness

```

```

C_ox = e_ox/t_ox          # oxide capacitance
V_thn = 0.7                # threshold voltage (device parameter)
Ldn = 0.08e-6
Leff = L - 2*Ldn

I_dp = I_ss/2 + 0.25*u_n*C_ox*(W/L)*V_id*np.sqrt(4*I_ss/(u_n*C_ox*(W/L)) -
→V_id**2)
I_dm = I_ss/2 - 0.25*u_n*C_ox*(W/L)*V_id*np.sqrt(4*I_ss/(u_n*C_ox*(W/L)) -
→V_id**2)

return I_dp, I_dm

```

## 2 Lecture 7 - gm/ID Design

### 2.1 Announcements

- Midterm exam available now, due February 21
  - 180-minute time limit, administered as a Canvas quiz
- Design Project Phase 1 posted, due Sunday March 7
  - PDF submission on Canvas

### 2.2 Week 7

### 2.3 Overview

- Last time...
  - MOS capacitance
  - Common source amplifier
  - Miller Effect
  - Zero Value Time Constant (ZVTC) analysis
  - Gain-bandwidth product
- Today...
  - CMOS amplifier design
  - Subthreshold MOS operation
  - $g_m/I_D$  design methodology


### 2.4 Amplifier design considerations

- Analog design involves compromises between
  - Speed (circuit bandwidth)
  - Noise (SNR)
  - Power dissipation (supply current)
  - Size (silicon area)
- Design typically begins with a target for one or more of these metrics
- Sometimes, one or more metrics may constitute a degree of freedom (e.g. no noise spec)

## 2.5 Transistor sizing methodology

- Other limitations/constraints apply, including supply voltage, input voltage range, and output swing
- These requirements need to be met while satisfying the core specifications (i.e. power and bandwidth)
- Every transistor should be sized with these targets in mind (i.e. no random selection of  $W/L$  values)
- Transistor sizes should ideally be determined with little to no “tweaking” in Cadence

## 2.6 Amplifier design example

 

- Specifications:

$$A(j0) \approx -g_{m1,2} r_{o2} || r_{o4} \quad (1)$$

$$\omega_{3dB} = \frac{1}{r_{o2} || r_{o4} C_L} \quad (2)$$

$$GBW = |A(j0)| \cdot \omega_{3dB} \approx \frac{g_{m1,2}}{C_L} \quad (3)$$


- Amplifier bandwidth/power tradeoff:

$$GBW = \frac{I_{SS}}{V_{OV1,2} \cdot C_L} = \frac{P_{diss}/V_{DD}}{V_{OV1,2} \cdot C_L} \quad (4)$$

- There is a tradeoff between power and bandwidth due to  $I_{SS}$  and  $C_L$  limitations

- If both are specified/constrained, design will be a process of optimization (e.g. maximize bandwidth under a given power constraint, or minimize power while meeting bandwidth spec)

## 2.7 Amplifier design example

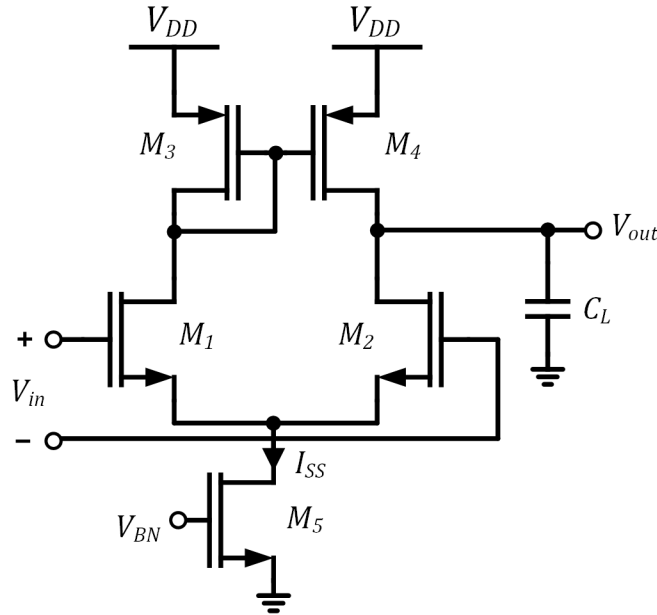

- Specifications:

$$GBW \approx \frac{g_{m1,2}}{C_L} \quad P_{diss} = I_{SS} \cdot V_{DD} \quad (5)$$

- Design:

$$g_{m1,2} \approx GBW \cdot C_L = \frac{I_{SS}}{V_{OV1,2}} \quad (6)$$

$$(7)$$

$$\left(\frac{W}{L}\right)_{1,2} = \frac{I_{SS}}{\mu_n C_{ox} V_{OV1,2}^2} \quad (8)$$


- $V_{DD}$ ,  $C_L$ , and  $P_{diss}$  are set by either specifications or technology limitations
- $M_{1,2}$  should be sized based on the required overdrive voltage
- Selection of  $I_{SS}$  and sizing of  $M_1$ ,  $M_2$  follows directly from specifications

## 2.8 Long-channel model limitations

- Unfortunately, modern “short-channel” devices do not obey long-channel equations

- Starting with these equations typically leads to an iterative, *simulate-and-repeat* process, which is counter to our goal of “no tweaking”
- We would like to
  - Follow a reasonably simple design approach requiring minimal hand analysis, and
  - Obtain accurate results with little to no iteration (i.e. right the first time)
- It turns out that this is largely possible through an approach called  $g_m/I_D$  design

## 2.9 Amplifier design, revisited

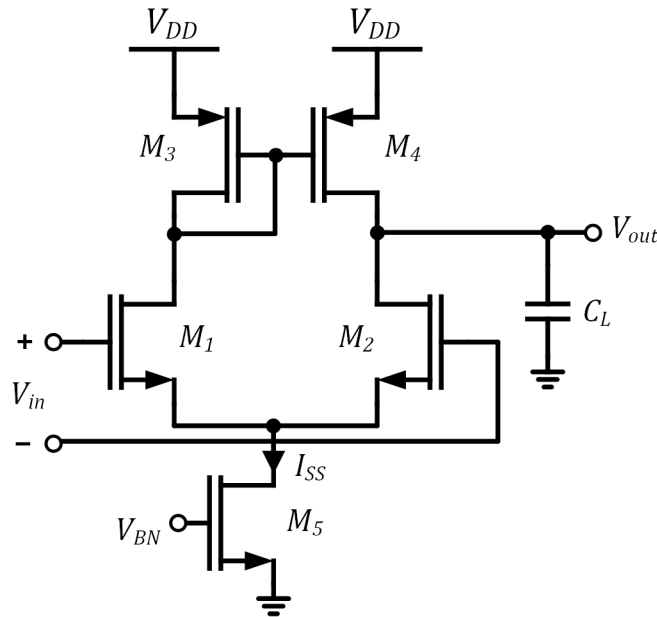

- Specifications:


$$GBW \approx \frac{g_{m1,2}}{C_L} \quad P_{diss} = I_{SS} \cdot V_{DD} \quad (9)$$

- Required value of  $g_m/I_D$ :

$$\frac{g_m}{I_D} \approx \frac{2 \cdot GBW \cdot C_L}{I_{SS}} = \frac{2}{V_{OV}} \quad (10)$$

- Viewing specifications in terms of transconductance efficiency ( $g_m/I_D$ ) provides a model- and operating region-agnostic approach to design and sizing
- However,  $g_m/I_D$  depends on process technology and operating region, making the simple square-law MOS model inaccurate in many cases
- From the above expression for  $g_m/I_D$ , it seems like we can just continue decreasing  $V_{OV}$  to obtain infinitely higher transconductance efficiency values!

## 2.10 Subthreshold MOS operation

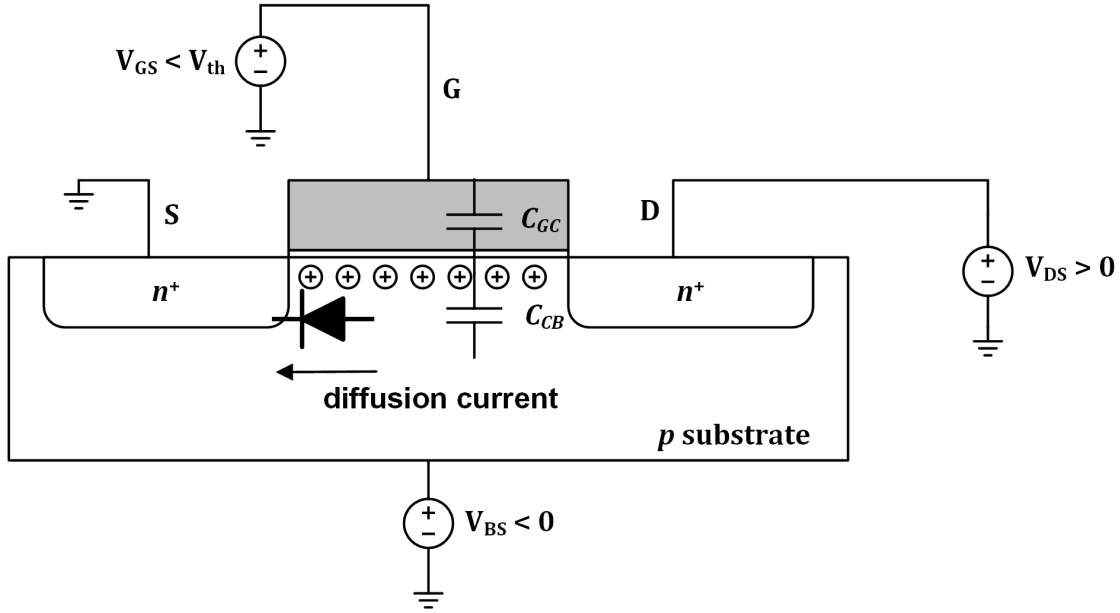

- Subthreshold drain current

$$I_D = I_S \exp \frac{V_{GS}}{\zeta V_T} \quad (11)$$

- where

$$\zeta = \frac{C_{GC} + C_{CB}}{C_{GC}} \quad (12)$$

- As  $V_{OV}$  decreases,  $V_{GS}$  becomes equal to/less than  $V_{th}$
- For  $V_{GS}$  values less than  $V_{th}$ , the bulk region under the gate has a high concentration of majority carriers (holes for NMOS)
- Increasing/decreasing the gate potential in this regime lowers/raises the potential barrier for diffusion of majority carriers between the S/B regions (this is similar to BJT operation)
- $\zeta$  is a process parameter, typically in the range 1.5 to 2

## 2.11 Subthreshold transconductance

- For subthreshold operation (also called weak inversion), transconductance is given as

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{\partial}{\partial V_{GS}} I_S \exp \frac{V_{GS}}{\zeta V_T} = \frac{I_S \exp \frac{V_{GS}}{\zeta V_T}}{\zeta V_T} = \boxed{\frac{I_D}{\zeta V_T}} \quad (13)$$

- This is an analogous expression to the transconductance of a BJT, with the exception of the  $\zeta$  term
- As in the square-law model, transconductance varies linearly with  $I_D$



- Both drain current and transconductance are in fact continuous functions of  $V_{GS}$ , and the models merely serve as approximations
- It should be noted that the accuracy of both square law and exponential models is poor for  $V_{GS} \approx V_{th}$

## 2.12 Transconductance efficiency (gm/ID)

- In saturation, the transconductance is given by

$$g_m = \frac{2I_D}{V_{OV}} \quad (14)$$

- From this we can define the transconductance efficiency, given by

$$\frac{g_m}{I_D} = \frac{2}{V_{OV}} \quad (15)$$


- For a MOS transistor in subthreshold, this becomes

$$\frac{g_m}{I_D} = \frac{1}{\zeta V_T} \quad (16)$$

- At room temperature (300K) for  $\zeta \approx 1.5$ , this is limited to approximately

$$\frac{g_m}{I_D} \approx 26S/A \quad (17)$$

## 2.13 gm/ID design example

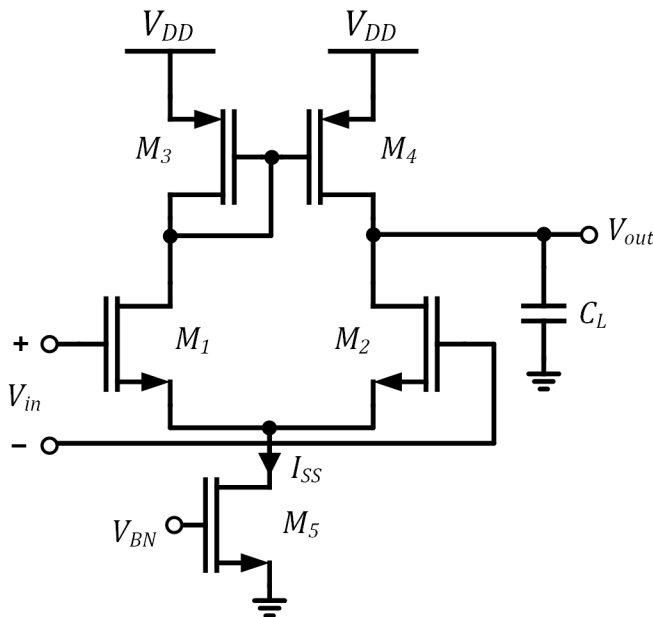

- Specifications:

$$V_{DD} = 2.5V \quad C_L = 10pF \quad P_{diss} = 320\mu W \quad GBW = 10MHz \quad (18)$$


- Design calculations:

$$I_{D1,2} = \frac{P_{diss}}{2V_{DD}} = 64\mu A \quad (19)$$

$$g_{m1,2} = 2\pi \cdot 10MHz \cdot 10pF = 630\mu S \quad (20)$$

$$\frac{g_m}{I_D} = \frac{630\mu S}{64\mu A} \approx 10V^{-1} \quad (21)$$

## 2.14 gm/ID current density chart

 

## 2.15 Input pair sizing



- The allowable current for  $M_{1,2}$  is based on the power dissipation spec:

$$I_{D1,2} = \frac{P_{diss}}{2V_{DD}} = 64\mu A \quad (22)$$


- The current density chart allows us to directly select  $W$  based on the target  $g_m/I_D$  and the target drain current  $I_{D1,2}$

$$W_{1,2} = \frac{I_{D1,2}}{I_D/W} = \frac{64\mu A}{2.6\mu A/\mu m} = 25.6\mu m \quad (23)$$

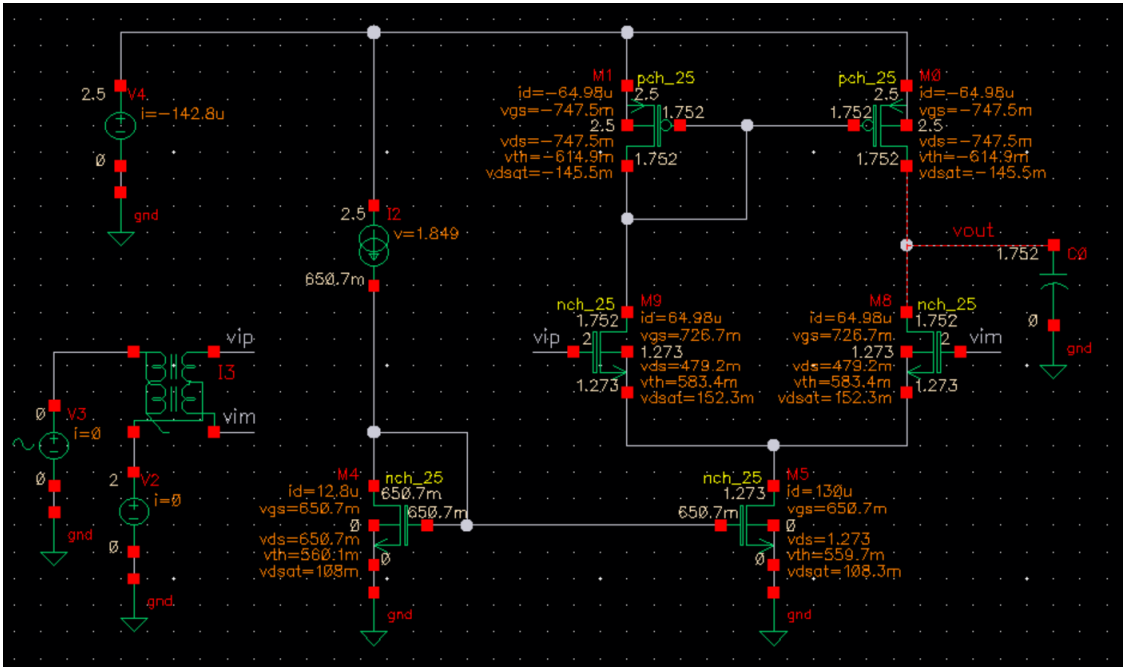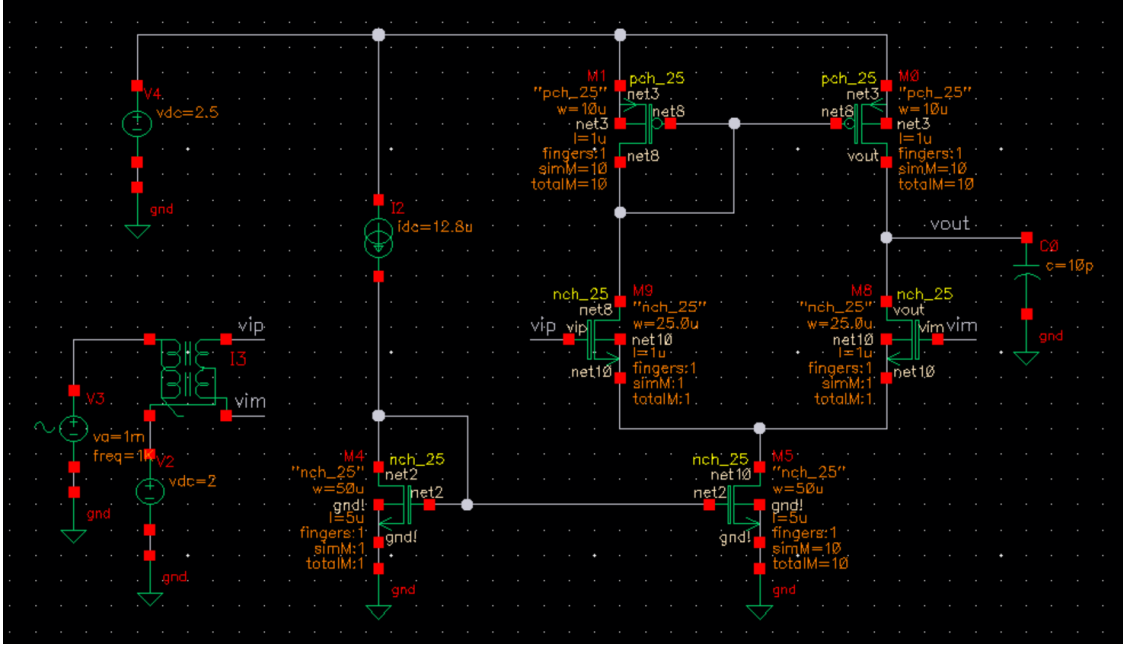- We can use the same approach to size bias devices in terms of  $V_{OV}$  with the corresponding charts (e.g.  $V_{OV}$  vs  $I_D/W$ )



## 2.16 Simulation results

 

## 2.17 $g_m/I_D$ design results

- Our design is essentially right on target, with little to no need for tweaking
- This result was achieved without using any of the long-channel equations
- Much less model uncertainty, since the model complexity is “built in” to the  $g_m/I_D$  chart generated by simulation
- $g_m/I_D$  design enables the designer to think in terms of transconductance efficiency and current density, improving intuition relative to an equation-based approach

## 2.18 General design flow

- Determine the required value(s) of  $g_m$ ,  $g_m r_o$ , or  $V_{OV}$  from design objectives (e.g. bandwidth, gain, output swing)
- Select channel length  $L$ 
  - Short channel  $\rightarrow$  high  $f_T$  (high speed)
  - Long channel  $\rightarrow$  high intrinsic gain, good matching
- Determine required value of  $g_m/I_D$ 
  - Large  $g_m/I_D \rightarrow$  low power or large signal swing (low  $V_{OV}$ )
  - Small  $g_m/I_D \rightarrow$  high speed, better linearity
- Determine  $I_D$  from  $g_m$  and  $g_m/I_D$
- Determine  $W$  from current density ( $I_D/W$ ) chart

## 2.19 Summary

- Analog CMOS design can (and should) be a systematic process
  - Specifications  $\rightarrow$  circuit architecture  $\rightarrow$  device currents/sizes

- The long-channel MOS model is inadequate for accurately predicting device behavior in short-channel CMOS technologies or at low current densities (subthreshold)
- $g_m/I_D$  design offers a unified approach that captures complex device model behavior while still allowing the use of simple expressions for making design decisions