

# 2021\_01\_13\_EE538\_Lecture2\_W2021

January 12, 2021

## 1 EE 538: Analog Integrated Circuit Design

### 1.1 Winter 2021

### 1.2 Instructor: Jason Silver

### 1.3 Python packages/modules

```
[37]: import matplotlib as mpl
from matplotlib import pyplot as plt
import numpy as np
from scipy import signal
%%matplotlib notebook

mpl.rcParams['font.size'] = 12
mpl.rcParams['legend.fontsize'] = 'large'

def plot_xy(x, y, xlabel, ylabel):
    fig, ax = plt.subplots(figsize=(10.0, 7.5));
    ax.plot(x, y, 'b');
    ax.grid();
    ax.set_xlabel(xlabel);
    ax.set_ylabel(ylabel);

def plot_xy2(x1, y1, x1label, y1label, x2, y2, x2label, y2label):
    fig, ax = plt.subplots(2, figsize = (10.0, 7.5));
    ax[0].plot(x1, y1, 'b');
    ax[0].set_ylabel(y1label)
    ax[0].grid()

    ax[1].plot(x2, y2, 'b');
    ax[1].set_xlabel(x1label)
    ax[1].set_xlabel(x2label);
    ax[1].set_ylabel(y2label);
    ax[1].grid();

    fig.align_ylabels(ax[:])
```

```

def plot_xlogy(x, y, xlabel, ylabel):
    fig, ax = plt.subplots(figsize=(10.0, 7.5));
    ax.semilogy(x, y, 'b');
    ax.grid();
    ax.set_xlabel(xlabel);
    ax.set_ylabel(ylabel);

def nmos_iv_sweep(V_gs, V_ds, W, L, lmda):
    u_n = 350 # electron mobility (device parameter)
    e_ox = 3.9*8.854e-12/100; # relative permittivity
    t_ox = 9e-9*100; # oxide thickness
    C_ox = e_ox/t_ox # oxide capacitance
    V_thn = 0.7 # threshold voltage (device parameter)
    V_ov = V_gs - V_thn
    Ldn = 0.08e-6
    Leff = L - 2*Ldn

    I_d = []

    for i in range(len(V_ds)):
        I_d.append(np.piecewise(V_ds[i], [V_ds[i] < V_ov, V_ds[i] >= V_ov],
                                [u_n*C_ox*(W/Leff)*(V_gs - V_thn - V_ds[i]/
→2)*V_ds[i]*(1+lmda*V_ds[i]) ,
                                0.5*u_n*C_ox*(W/Leff)*(V_gs -
→V_thn)**2*(1+lmda*V_ds[i])]))

    return np.array(I_d)

def pmos_iv_sweep(V_sg, V_sd, W, L, lmda):
    u_p = 100 # electron mobility (device parameter)
    e_ox = 3.9*8.854e-12/100; # relative permittivity
    t_ox = 9e-9*100; # oxide thickness
    C_ox = e_ox/t_ox # oxide capacitance
    V_thp = -0.8 # threshold voltage (device parameter)
    V_ov = V_sg - np.abs(V_thp)
    Ldp = 0.09e-6
    Leff = L - 2*Ldp

    I_d = []

    for i in range(len(V_sd)):
        I_d.append(np.piecewise(V_sd[i], [V_sd[i] < V_ov, V_sd[i] >= V_ov],
                                [u_p*C_ox*(W/Leff)*(V_sg - np.abs(V_thp) - V_sd[i]/
→2)*V_sd[i]*(1+lmda*V_sd[i]) ,
                                0.5*u_p*C_ox*(W/Leff)*(V_sg - np.
→abs(V_thp))**2*(1+lmda*V_sd[i])]))

```

```

return np.array(I_d)

def nmos_iv_sat(V_gs, V_ds, W, L, lmda):
    u_n = 350 # electron mobility (device parameter)
    e_ox = 3.9*8.854e-12/100; # relative permittivity
    t_ox = 9e-9*100; # oxide thickness
    C_ox = e_ox/t_ox # oxide capacitance
    V_thn = 0.7 # threshold voltage (device parameter)
    V_ov = V_gs - V_thn
    Ldn = 0.08e-6
    Leff = L - 2*Ldn

    I_d = 0.5*u_n*C_ox*(W/Leff)*(V_gs - V_thn)**2*(1+lmda*V_ds)

    return I_d

```

## 2 Lecture 2 - Single-Stage MOS Amplifiers


### 2.1 Week 2

- Chapter 2 of Razavi (basic MOS physics)
  - Review: DC small signal model (2.4.3)
- Chapter 3 of Razavi (single-stage amplifiers)
- Chapter 5 of Razavi (current mirrors)
  - Section 5.1 Basic Current Mirrors


### 2.2 Overview

- Last time...
  - MOSFET drain current a product of vertical ( $V_{GS}$ ) and lateral ( $V_{DS}$ ) electric fields
  - MOS behaves as a resistor in triode ( $V_{DS} \ll V_{GS} - V_{TH}$ ) and a current source in saturation ( $V_{DS} > V_{GS} - V_{TH}$ )
  - Small-signal model obtained by linearizing MOS behavior about a DC operating point (i.e. specific value of  $V_{GS} = V_{GS0}$ )
- Today...
  - Small signal model, cont.
  - PMOS transistors
  - Common source amplifier
    - \* Passive load
    - \* Active load
  - Basic current mirror

## 2.3 First-order MOS model summary

 

## 2.4 DC small-signal model

 


$$I_D = f(V_{GS}, V_{DS})$$

$$g_m = \frac{2I_{D0}}{V_{OV}} \quad r_o = \frac{1}{g_{ds}} = \frac{1}{\lambda I_{D0}}$$

- Small-signal model replaces nonlinear  $I_D(V_{GS}, V_{DS})$  with linear parameters  $g_m$  and  $r_o$  that enable the use of linear circuit analysis techniques
- *Important:* All DC voltages become AC ground in the small-signal model


## 2.5 PMOS transistor

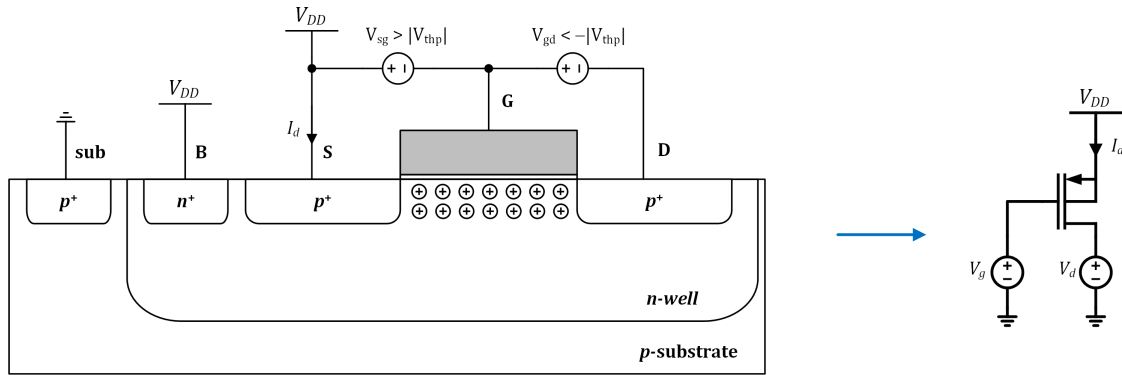

- In CMOS processes, PMOS transistors are produced in the same substrate as NMOS
- To operate in saturation, the following requirements must be satisfied:
  - $V_{sg} > |V_{thp}|$
  - $V_{sd} > V_{sg} - |V_{thp}|$
- The saturation current for a PMOS transistor is thus given by

$$I_d = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{sg} - |V_{thp}|)^2 (1 + \lambda V_{sd}) \quad (1)$$

## 2.6 High-gain amplifier design

 

$$G = \frac{V_{out}}{V_{in}} = \frac{A_v}{1 + \beta A_v} \quad (2)$$


$$\beta = \frac{R_1}{R_1 + R_2} \quad (3)$$

- if  $\beta A_v \gg 1$ ,

$$G = \frac{A_v}{1 + \beta A_v} \rightarrow \frac{1}{\beta} \quad (4)$$

- High-gain amplifiers are used to desensitize transfer functions to temperature- and manufacturing-dependent physical parameters (e.g.  $g_m$  and  $r_o$ )
- Typical values of  $A_v$  for opamps are  $100 - 140dB$  ( $100,000 - 10,000,000V/V$ )
- High *open-loop* gain ( $A_v$ )  $\rightarrow$  precise *closed-loop* gain ( $G$ )
- For this reason, when designing CMOS amplifiers (i.e. opamps and OTAs) substantial emphasis is placed on achieving high open-loop gain

## 2.7 Common-source amplifier

 

$$I_d = \frac{1}{2} \mu \cdot C_{ox} \cdot \frac{W}{L} (V_i - V_{th})^2 (1 + \lambda V_o) \quad (5)$$

$$V_o = V_{DD} - I_d \cdot R_D \quad (6)$$

- The common-source amplifier is an exemplary model of how we achieve gain in analog circuits:
  - Change in the output current  $\Delta I_d$  is realized (primarily) by a change in the input voltage  $\Delta V_i$  and the voltage-current relationship of the device
  - Output voltage changes as the result of  $\Delta I_d$  flowing through the output resistance of the circuit (in this case,  $R_D$ )


## 2.8 Output voltage minimum/maximum (swing)

- For the maximum voltage, when  $V_o = V_{DD}$ , current no longer flows through  $R_D$  and changes in the input cannot effect changes in the output
- For the minimum, to ensure the transistor remains in saturation  $V_o$  should be greater than the overdrive voltage,  $V_i - V_{th}$
- The valid range of output voltages is thus

$$V_i - V_{th} < V_o < V_{DD} \quad (7)$$


- Assuming signals swing symmetrically above and below the operating point, we can maximize use of the output swing by selecting  $R_D$  and  $I_D$  to an output operating point at the output of  $V_o = V_{DD}/2$

## 2.9 Small-signal model

 


- $V_{DD}$  is a DC (constant) voltage, making it an AC (small-signal) ground
- $r_o$  and  $R_D$  appear in parallel in the small-signal model

## 2.10 MOS amplifier analysis

 

- Voltage gain in transistor-based circuits is *almost always* realized as the product of a transconductance  $G_m$  and a small-signal resistance  $R_o$
- Analysis approach: Use Norton analysis to determine the parameters  $G_m$  and  $R_o$  using the small signal model
  - Find the short-circuit current  $i_{sc}$  to determine  $G_m = i_{sc} / v_{in}$
  - The output resistance  $R_o$  is determined by setting  $v_{in} = 0$ , applying a test voltage to the output, and finding the expression for the resulting current
 
## 2.11 Common-source Norton model ( $G_m$ )




- To determine  $G_m$  in the Norton model, short the output terminals and measure  $i_{sc}$
- Due to the short circuit, no current flows through  $r_o$  or  $R_D$
- $G_m$  is determined by taking the ratio of  $i_{sc}$  to  $v_i$ :

$$G_m = \frac{i_{sc}}{v_i} = \frac{g_m \cdot v_i}{v_i} = g_m \quad (8)$$

- Thus, in the case of the common-source amplifier,  $G_m = g_m$
 
## 2.12 Common-source Norton model ( $R_o$ )



- To determine  $R_o$ , apply a test voltage  $v_t$  between the output terminals and measure  $i_t$
- Here we can see that  $i_t$  is given by

$$i_t = v_t \cdot \left( \frac{1}{r_o} + \frac{1}{R_D} \right) \quad (9)$$

- Thus,  $R_o$  is just the parallel combination of  $r_o$  and  $R_D$ :

$$R_o = \frac{v_t}{i_t} = \left( \frac{1}{r_o} + \frac{1}{R_D} \right)^{-1} = \boxed{r_o || R_D} \quad (10)$$

## 2.13 Relative magnitudes of $R_D$ and $r_o$

- Output resistance  $r_o$  is given by the expression

$$r_o \approx \frac{1}{\lambda I_{D0}} \quad (11)$$

- Typical drain resistance  $R_D$  can be expressed as (assumes output DC operating point of  $V_{DD}/2$ , which allows for maximal output signal swing)

$$R_D \approx \frac{V_{DD}}{2I_{D0}} \quad (12)$$

- For  $V_{DD} = 3V$  and  $\lambda = 0.1V^{-1}$ ,  $r_o \approx 7 \times R_D$
- Thus, for the common-source amplifier,

$$\boxed{A_v = -g_m(r_o || R_D) \approx -g_m \cdot R_D} \quad (13)$$

## 2.14 Maximum gain with $R_D$

- What is the maximum gain that can be achieved with a passive (resistive) load?

$$A_v \approx -g_m \cdot R_D = -\frac{2I_{D0}}{V_{ov}} R_D \quad (14)$$


- Assuming an operating point for the output voltage of  $V_{DD}/2$ , the gain is given by



$$|A_v| \approx \frac{2 \cdot V_{DD}/2}{R_D \cdot V_{ov}} \cdot R_D = \frac{V_{DD}}{V_{ov}} \quad (15)$$

- Assuming  $V_{DD} = 3V$  and  $V_{ov} = 150mV$ , this limits the gain to approximately  $20V/V$
- This is generally too low to be useful in building an opamp
- How do we increase gain?

## 2.15 MOS DC model (intrinsic gain)

 

$$g_m = \frac{2I_{D0}}{V_{OV}} \quad (16)$$

$$r_o = \frac{1}{g_{ds}} = \frac{1}{\lambda I_{D0}} \quad (17)$$

$$\left| \frac{v_{ds}}{v_{gs}} \right| = \frac{g_m}{g_{ds}} = \frac{2}{\lambda V_{OV}} \quad (18)$$

- Recall that the intrinsic gain of the transistor is given by the product of  $g_m$  and  $r_o$
- $g_m$  increases linearly with drain current, while  $r_o$  is inversely dependent, keeping their product constant
- What is a typical value for  $g_m r_o$ ?


## 2.16 Intrinsic gain

- In our Level 1 “process”  $\lambda_n = 0.1V^{-1}$
- In order to maximize signal swing, we want to use a relatively low overdrive voltage ( $V_{ov} = V_{GS} - V_{th}$ )
- Assuming a gate bias of  $V_{GS} = 0.9V$  (for example), the intrinsic gain is given as

$$g_m r_o \approx \frac{2}{\lambda V_{ov}} = \frac{2}{0.1V^{-1} \times 200mV} = 100V/V \quad (19)$$


- This is  $5\times$  the theoretical gain with a resistive load
- How can we can advantage of intrinsic gain to build amplifiers with gains approaching/exceeding  $100dB$ ?

## 2.17 Common-source with active load

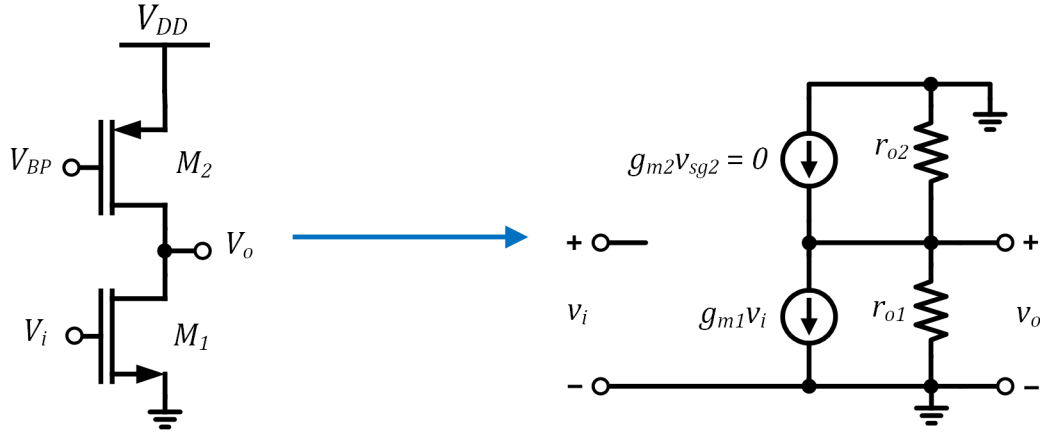

- We can increase the gain of the common-source stage by replacing the resistor  $R_D$  with a PMOS transistor in saturation
- This is referred to as an *active* load, since it replaces a passive device (resistor) with an active one (transistor)
- The bias voltage  $V_{BP}$  sets the DC operating point ( $g_{m1,2}$  and  $r_{o1,2}$ ) of the amplifier stage by controlling the drain currents of  $M_1$  and  $M_2$
- Because both  $V_S$  and  $V_G$  of  $M_2$  are DC voltages, its transconductance current is zero in the small-signal model

## 2.18 Small-signal gain

 

- In this circuit,  $M_1$  functions as a transconductor and  $M_2$  behaves as a resistance
- The small-signal gain expression is identical to that of the passive load, with  $R_D$  replaced by  $r_{o2}$ :

$$A_v = \frac{v_o}{v_i} = -g_{m1} \cdot (r_{o1} || r_{o2}) \quad (20)$$

- If we make the (somewhat dubious) assumption that  $r_{op} = r_{on} = r_o$ , we can relate the gain of the active load stage to the MOSFET's intrinsic gain:

$$A_v = \frac{v_o}{v_i} = -g_{m1} \cdot (r_{o1} || r_{o2}) \approx -\frac{g_m \cdot r_o}{2} \quad (21)$$

- In practice  $r_{on} \neq r_{op}$ , but are of the same order of magnitude

## 2.19 Magnitude of the gain

- Recall that the gain of the common-source stage with a passive load ( $R_D$ ) is

$$A_v = -g_m(r_o || R_D) \approx -g_m \cdot R_D \quad (22)$$

- For a nominal DC output voltage of  $V_{DD}/2$  (i.e. the DC operating point), this is

$$|A_v| \approx \frac{2 \cdot V_{DD}/2}{R_D \cdot V_{ov}} \cdot R_D = \frac{V_{DD}}{V_{ov}} \leq 20V/V \quad (23)$$

- For the active-load stage, the gain is given by

$$A_v = \frac{v_o}{v_i} = -g_{m1} \cdot (r_{o1} || r_{o2}) \quad (24)$$

- Using our Level 1 process parameters, this becomes

$$A_v = -g_{m1} \cdot (r_{o1} || r_{o2}) = -g_{m1} \cdot r_{o1} \frac{r_{o2}}{r_{o1} + r_{o2}} \approx 33V/V \quad (25)$$

- This is an improvement, but still fairly low. We'll discuss how to increase this soon...

## 2.20 Output voltage range

- When  $V_o$  is at its maximum value,  $M_2$  still needs to be in saturation to operate as a high-resistance load, requiring

$$V_o < V_{DD} - V_{BP} - |V_{thp}| \quad (26)$$

- Similarly,  $M_1$  needs to remain in saturation, setting the lower bound on  $V_o$  as

$$V_o > V_i - V_{th} \quad (27)$$

- The valid range of output voltages is thus

$$V_i - V_{thn} < V_o < V_{DD} - V_{BP} - |V_{thp}| \quad (28)$$

- Again to maximize use of this range we would like to set the operating point of  $V_o$  to approximately  $V_{DD}/2$
- How do we set the operating point?


```
[20]: def plot_cs_op_point(V_DD, V_BP, V_GS1, V_out):
    I_d1 = nmos_iv_sweep(V_GS1, V_out, 100, 1, 0.1)
    I_d2 = pmos_iv_sweep(V_DD-V_BP, V_DD-V_out, 200, 1, 0.2)

    fig, ax = plt.subplots(figsize=(10.0, 7.5))
    ax.plot(V_out, 1e6*I_d1, label=r'$I_{d,NMOS}$', color='blue')
    ax.plot(V_out, 1e6*I_d2, label=r'$I_{d,PMOS}$', color='red')
    ax.set_xlabel(r'$V_{out}$ [V]')
```


```
ax.set_ylabel(r'$I_{d}$ [\mu A]$')
ax.legend()
ax.grid()
```

- Because  $I_{D1} = I_{D2}$ , the point at which the drain current curves intersect constitutes the operating point of the circuit
- For a nominal (DC) input voltage of  $0.86V$ , both transistors are approximately in the middle of their saturation ranges and the output voltage is  $\sim V_{DD}/2$
- However, if  $V_{GS1}$  is changed slightly, the resulting operating point can place either  $M_1$  or  $M_2$  in triode, drastically decreasing the gain
- Feedback is required to stabilize the output DC voltage at a desired value (more on this later)
 
```
[36]: V_DD = 3
      V_BP = 2
      V_GS1 = .9
      V_out = np.arange(0,3,step=0.01)
      plot_cs_op_point(V_DD, V_BP, V_GS1, V_out)
```



## 2.21 Common-source biasing

 


- If the output voltage is maintained such that both  $M_1$  and  $M_2$  remain in saturation, the gain is determined by

$$A_v = \frac{v_o}{v_i} = -g_{m1} \cdot r_{o1} || r_{o2} \quad (29)$$

- where  $g_{m1} = 2I_{D1}/V_{OV1}$ ,  $r_{o1} = 1/\lambda_n I_{D1}$ ,  $r_{o2} = 1/\lambda_p I_{D2}$ , and  $I_{D1} = I_{D2}$
- $I_{D2}$  ( $I_{D1}$ ) constitutes the DC operating point of the circuit, and is often referred to as the “bias current”
- How do we control  $I_{D2}$ ?

## 2.22 Basic current mirror

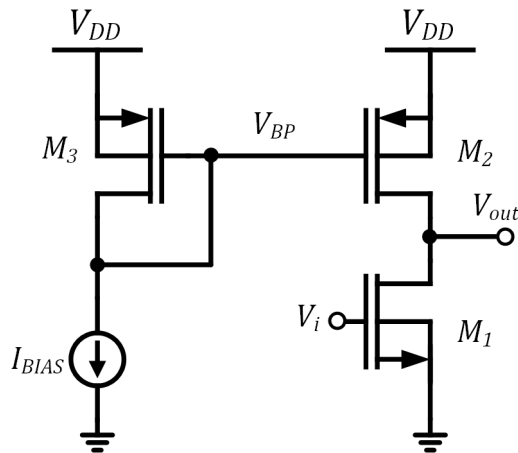

- Assuming  $\lambda_p = 0$ , if  $(W/L)_2 = (W/L)_3$ ,


$$I_{D1} = I_{D2} = I_{D3} = I_{BIAS} \quad (30)$$

- Hence,

$$g_{m1} = \frac{2I_{BIAS}}{V_{OV}}, \quad r_{o1} = \frac{1}{\lambda_n I_{BIAS}}, \quad r_{o2} = \frac{1}{\lambda_p I_{BIAS}} \quad (31)$$

- A “diode-connected” transistor ( $M_3$  in the figure) converts a current ( $I_{BIAS}$ ) into a voltage ( $V_{BP}$ ) based on the relation
- Current biasing in this manner allows us to control the small-signal performance of the circuit by designing  $I_{BIAS}$  to achieve specific goals (e.g. gain, bandwidth, noise)

### 2.23 Current mirror operation

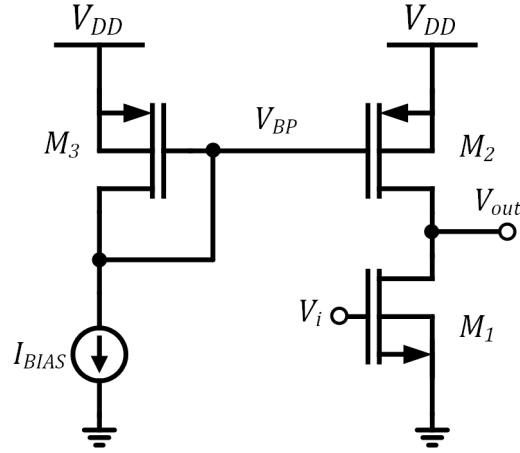

- Again, assuming  $\lambda_p = 0$

$$V_{SG3} = |V_{thp}| + \sqrt{\frac{2 \cdot I_{BIAS}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_3}} \quad (32)$$

- The common-source bias current is thus


$$I_{D1} = I_{D2} = \frac{1}{2} \mu \cdot C_{ox} \cdot \frac{W}{L} (V_{DD} - V_{BP} - |V_{thp}|)^2 \quad (33)$$

- The “diode” connection (gate and drain shorted together) ensures  $M_3$  is always in saturation, since

$$V_{SG} = V_{SD} > V_{SG} - |V_{thp}| \quad (34)$$

- Because  $M_2$  and  $M_3$  share gate and source connections,  $M_2$  “mirrors” (i.e. copies)  $M_3$ ’s current
- However, we have ignored the fact that  $V_{SD2}$  is not necessarily equal to  $V_{SD3}$
- How do  $I_{D1}$ ,  $I_{D2}$  vary with  $V_{out}$ ?

## 2.24 Finite output resistance

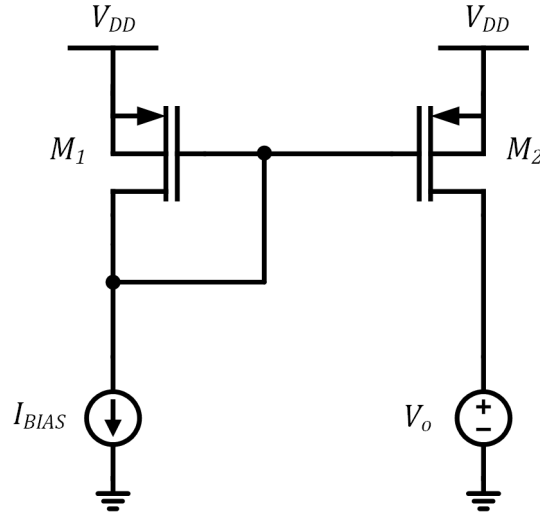

- Considering the effect of channel-length modulation on  $M_2$ 's drain current gives

$$I_{D2} = \frac{1}{2} \mu \cdot C_{ox} \cdot \frac{W}{L} (V_{DD} - V_{BP} - |V_{thp}|)^2 [1 + \lambda(V_{DD} - V_o)] \quad (35)$$

- To assess the dependence of  $I_{D2}$  on  $V_o$ , we can take the derivative

$$\frac{\partial I_{D2}}{\partial V_o} = \frac{1}{r_{o2}} \quad (36)$$

- The purpose of  $M_2$  is to provide current for the common-source stage
- The output resistance of the current mirror captures the dependence of  $I_{D2}$ , which determines *how* effectively it operates as a current source
- It turns out then that the same factor limiting voltage gain in the common-source stage limits the precision of a current mirror: *output resistance*
- How can we increase output resistance and, as a result, gain?
- More on this next time...

## 2.25 Summary

- High gain in operational amplifiers (Opamps) and operational *transconductance* amplifiers (OTAs) is achieved using (one or more) structures similar in form to the common-source stage
  - Voltage gain is realized as the product of a transconductance ( $G_m$ ) and a resistance ( $R_o$ )
- Active loads enable higher values of  $R_o$ , and thus higher gain, than passive loads
- Current biasing allows us to precisely define the critical small-signal parameters ( $g_m$ ,  $r_o$ ) that determine circuit performance
- Finite MOS output resistance limits both gain and the precision of current mirrors
- Next time, we will look at how to build both better current mirrors and voltage amplification stages