

2021_02_24_EE538_Lecture8_W2021

February 23, 2021

1 EE 538: Analog Integrated Circuit Design

1.1 Winter 2021

1.2 Instructor: Jason Silver

1.3 Python packages/modules

```
[17]: import matplotlib as mpl
from matplotlib import pyplot as plt
import numpy as np
from scipy import signal
%%matplotlib notebook

mpl.rcParams['font.size'] = 12
mpl.rcParams['legend.fontsize'] = 'large'

def plot_xy(x, y, xlabel, ylabel):
    fig, ax = plt.subplots(figsize=(10.0, 7.5));
    ax.plot(x, y, 'b');
    ax.grid();
    ax.set_xlabel(xlabel);
    ax.set_ylabel(ylabel);

def plot_xy2(x1, y1, x1label, y1label, x2, y2, x2label, y2label):
    fig, ax = plt.subplots(2, figsize = (10.0, 7.5));
    ax[0].plot(x1, y1, 'b');
    ax[0].set_ylabel(y1label)
    ax[0].grid()

    ax[1].plot(x2, y2, 'b');
    ax[1].set_xlabel(x1label)
    ax[1].set_xlabel(x2label);
    ax[1].set_ylabel(y2label);
    ax[1].grid();

    fig.align_ylabels(ax[:])
```

```

def plot_x2y(x, y1, y2, xlabel, ylabel, y1label, y2label):

    fig, ax = plt.subplots(figsize=(10.0, 7.5));
    ax.plot(x, y1, 'b')
    ax.plot(x, y2, 'r')
    ax.legend( [y1label,y2label] ,loc='upper center', ncol=5, fancybox=True,
               shadow=True, bbox_to_anchor=(0.5,1.1))
    ax.grid()
    ax.set_xlabel(xlabel)
    ax.set_ylabel(ylabel)

def plot_xy3(x, y1, y2, y3, xlabel, y1label, y2label, y3label):
    fig, ax = plt.subplots(3, figsize=(10.0,7.5))

    ax[0].plot(x, y1)
    ax[0].set_ylabel(y1label)
    ax[0].grid()

    ax[1].plot(x, y2)
    ax[1].set_ylabel(y2label)
    ax[1].grid()

    ax[2].plot(x, y3)
    ax[2].set_ylabel(y3label)
    ax[2].set_xlabel(xlabel)
    ax[2].grid()

def plot_xlogy(x, y, xlabel, ylabel):
    fig, ax = plt.subplots(figsize=(10.0, 7.5));
    ax.semilogy(x, y, 'b');
    ax.grid();
    ax.set_xlabel(xlabel);
    ax.set_ylabel(ylabel);

def plot_logxy2(x1, y1, x2, y2, x1label, y1label, x2label, y2label):
    fig, ax = plt.subplots(2, figsize = (10.0, 7.5));
    ax[0].semilogx(x1, y1, 'b');
    ax[0].set_ylabel(y1label)
    ax[0].grid()

    ax[1].semilogx(x2, y2, 'b');
    ax[1].set_xlabel(x1label)
    ax[1].set_xlabel(x2label);
    ax[1].set_ylabel(y2label);
    ax[1].grid();

    fig.align_ylabels(ax[:])

```

```

def nmos_iv_sweep(V_gs, V_ds, W, L, lmda):
    u_n = 350 # electron mobility (device parameter)
    e_ox = 3.9*8.854e-12/100; # relative permittivity
    t_ox = 9e-9*100; # oxide thickness
    C_ox = e_ox/t_ox # oxide capacitance
    V_thn = 0.7 # threshold voltage (device parameter)
    V_ov = V_gs - V_thn
    Ldn = 0.08e-6
    Leff = L - 2*Ldn

    I_d = []

    for i in range(len(V_ds)):
        I_d.append(np.piecewise(V_ds[i], [V_ds[i] < V_ov, V_ds[i] >= V_ov],
                                [u_n*C_ox*(W/Leff)*(V_gs - V_thn - V_ds[i]/
→2)*V_ds[i]*(1+lmda*V_ds[i]) ,
                                0.5*u_n*C_ox*(W/Leff)*(V_gs -
→V_thn)**2*(1+lmda*V_ds[i])]))

    return np.array(I_d)

def pmos_iv_sweep(V_sg, V_sd, W, L, lmda):
    u_p = 100 # electron mobility (device parameter)
    e_ox = 3.9*8.854e-12/100; # relative permittivity
    t_ox = 9e-9*100; # oxide thickness
    C_ox = e_ox/t_ox # oxide capacitance
    V_thp = -0.8 # threshold voltage (device parameter)
    V_ov = V_sg - np.abs(V_thp)
    Ldp = 0.09e-6
    Leff = L - 2*Ldp

    I_d = []

    for i in range(len(V_sd)):
        I_d.append(np.piecewise(V_sd[i], [V_sd[i] < V_ov, V_sd[i] >= V_ov],
                                [u_p*C_ox*(W/Leff)*(V_sg - np.abs(V_thp) - V_sd[i]/
→2)*V_sd[i]*(1+lmda*V_sd[i]) ,
                                0.5*u_p*C_ox*(W/Leff)*(V_sg - np.
→abs(V_thp))**2*(1+lmda*V_sd[i])]))

    return np.array(I_d)

def nmos_iv_sat(V_gs, V_ds, W, L, lmda):
    u_n = 350 # electron mobility (device parameter)
    e_ox = 3.9*8.854e-12/100; # relative permittivity
    t_ox = 9e-9*100; # oxide thickness

```

```

C_ox = e_ox/t_ox          # oxide capacitance
V_thn = 0.7                # threshold voltage (device parameter)
V_ov = V_gs - V_thn
Ldn = 0.08e-6
Leff = L - 2*Ldn

I_d = 0.5*u_n*C_ox*(W/Leff)*(V_gs - V_thn)**2*(1+lmda*V_ds)

return I_d

def nmos_diff_pair(V_id, I_ss, R_D, W, L, V_dd):
    u_n = 350              # electron mobility (device parameter)
    e_ox = 3.9*8.854e-12/100; # relative permittivity
    t_ox = 9e-9*100;       # oxide thickness
    C_ox = e_ox/t_ox        # oxide capacitance
    V_thn = 0.7             # threshold voltage (device parameter)
    Ldn = 0.08e-6
    Leff = L - 2*Ldn

    I_dp = I_ss/2 + 0.25*u_n*C_ox*(W/L)*V_id*np.sqrt(4*I_ss/(u_n*C_ox*(W/L)) - V_id**2)
    I_dm = I_ss/2 - 0.25*u_n*C_ox*(W/L)*V_id*np.sqrt(4*I_ss/(u_n*C_ox*(W/L)) - V_id**2)

    return I_dp, I_dm

```

2 Lecture 8 - Stability and Frequency Compensation

2.1 Announcements

- Design Project Phase 1 posted, due Sunday March 7
 - PDF submission on Canvas
- Design Project Phase 2 will be posted soon


2.2 Week 8

2.3 Overview

- Last time...
 - CMOS amplifier design
 - Subthreshold MOS operation
 - g_m/I_D design methodology
- Today...
 - Feedback
 - Stability definition and criteria (Bode/root locus)
 - Damping ratio and phase margin
 - Mirror poles


- Compensation of two-stage amplifiers

2.4 Negative feedback

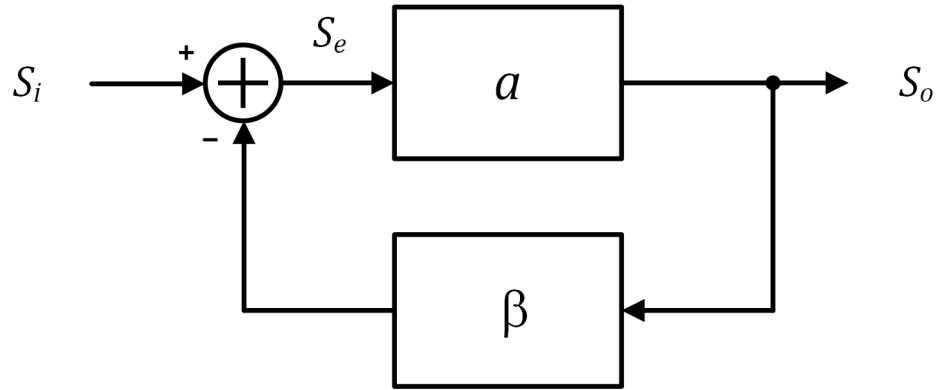

- Negative feedback loop processes the error $S_i(s) - \beta \cdot S_o(s)$
- If the magnitude of a is large, the error is minimized, i.e. $S_i(s) - \beta \cdot S_o(s) \rightarrow 0$
- In this sense, negative feedback “desensitizes” the transfer function to the open-loop gain a

2.5 Non-inverting amplifier

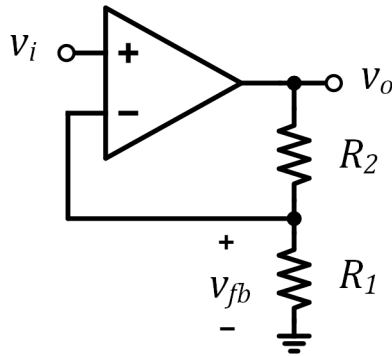


$$a = A_0 \quad (1)$$

$$\beta = \frac{R_1}{R_1 + R_2} \quad (2)$$

$$\frac{v_o}{v_i} = \frac{A_0}{1 + \beta A_0} \quad (3)$$

- A fraction of the output voltage (set by β) is fed back to the inverting input and the error voltage is processed by the amplifier
- Open-loop gain specification is determined by precision requirements (application-dependent)
- Exact value of DC gain A_0 is unimportant as long as it's “large enough”

2.6 Gain-bandwidth product

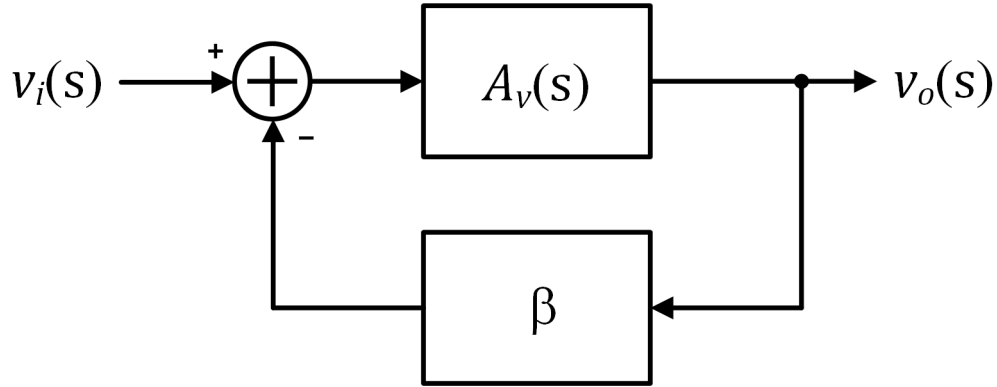

$$G(s) = \frac{v_o(s)}{v_i(s)} = \frac{A_v(s)}{1 + \beta A_v(s)} \quad (4)$$

$$A_v(s) = \frac{A_0}{1 + s/\omega_0} \quad (5)$$

$$GBW = A_0 \omega_0 \quad (6)$$

- Assuming dominant-pole behavior, we can readily assess the effect of negative feedback on frequency response
- A_0 is the DC gain of the *open-loop* amplifier, and ω_0 is the dominant pole frequency (i.e. 3dB bandwidth)
- To determine the frequency response of the closed-loop system, we substitute the frequency-dependent expression for $A_v(s)$ into the closed-loop gain expression

$$G(s) = \frac{A_v(s)}{1 + \beta A_v(s)} = \frac{A_0}{1 + s/\omega_0 + \beta A_0} = \frac{\frac{A_0}{1 + \beta A_0}}{1 + \frac{s}{\omega_0(1 + \beta A_0)}} \quad (7)$$

- Solving for the closed-loop pole frequency gives

$$\omega'_0 = \omega_0 \cdot (1 + \beta A_0) \quad (8)$$

```
[8]: def plot_CL_freq(A_dB, f_t, betas, w):
    A_0 = 10**(A_dB/20)
    f_3dB = f_t/A_0
    w_0 = f_3dB*2*np.pi
    A_s = np.array([])

    fig, axs = plt.subplots(2, figsize=(10.0, 8.0))
    for b in betas:
        Av_cl = signal.TransferFunction([A_0], [1/w_0, 1 + b*A_0])
        w, mag, phase = Av_cl.bode(w=w)          # rad/s, dB, degrees
```

```

f = w/2/np.pi

# Plot the frequency response for multiple values of beta
fig.suptitle('Opamp Closed-Loop Frequency Response')
axs[0].semilogx(f, mag)
axs[0].grid()
axs[0].set_ylabel('Magnitude [dB]')
axs[1].semilogx(f, phase)
axs[1].grid()
axs[1].set_ylabel('Phase [deg]')
axs[1].set_xlabel('Frequency [Hz]')
fig.align_ylabels(axs[:])


def plot_CL_step(A_dB, f_t, betas, w):
    A_0 = 10**(A_dB/20)
    f_3dB = f_t/A_0
    w_0 = f_3dB*2*np.pi
    A_s = np.array([])

    fig, axs = plt.subplots(2, figsize=(10.0, 8.0))
    for b in betas:
        Av_cl = signal.TransferFunction([A_0], [1/w_0, 1 + b*A_0])
        tin = np.linspace(0, 20e-6, 100)
        u_step = np.concatenate( (0, np.ones(99)), axis=None)
        tout, vout = signal.step(Av_cl, X0=None, T=tin)

        # Plot the step response for multiple values of beta
        fig.suptitle('Opamp Closed-Loop Step Response')
        axs[0].plot(1e6*tout, b*vout)
        axs[0].grid()
        axs[0].set_ylabel(r'$\beta V_o$ [V]')
        axs[1].plot(1e6*tin, u_step)
        axs[1].grid()
        axs[1].set_ylabel('Input Voltage [V]')
        axs[1].set_xlabel('Time [$\mu s$]')
        fig.align_ylabels(axs[:])

```

2.7 Gain-bandwidth (Bode)

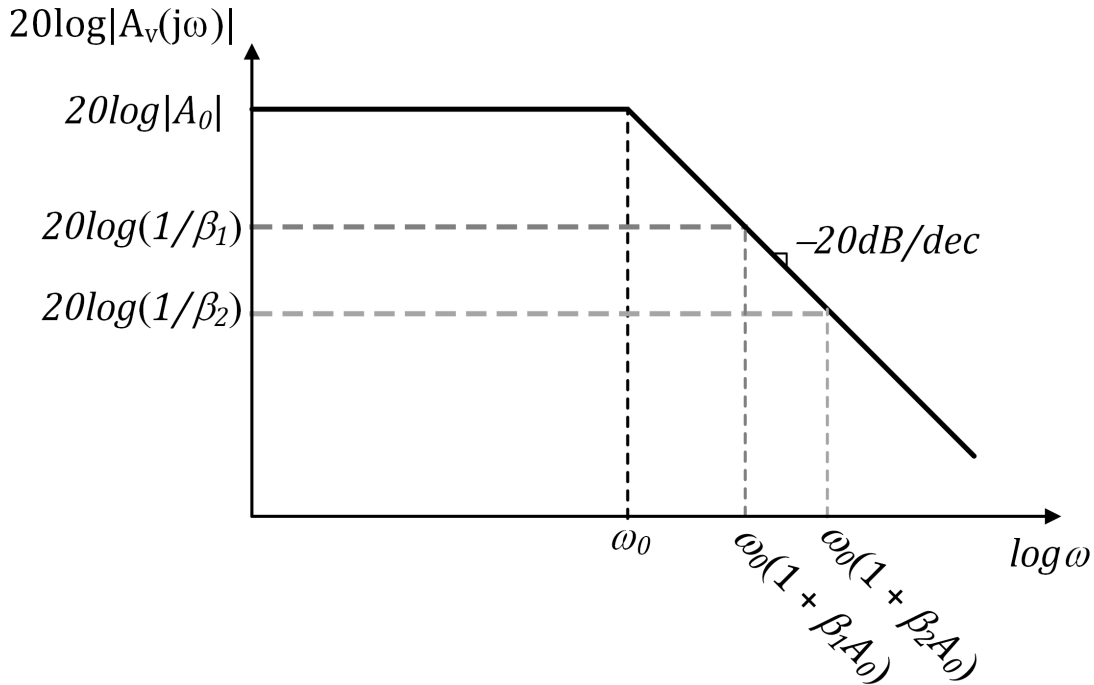

$$A_v(s) = \frac{A_0}{1 + s/\omega_0} \quad (9)$$


$$G(s) = \frac{\frac{A_0}{1 + \beta A_0}}{1 + \frac{s}{\omega_0(1 + \beta A_0)}} \quad (10)$$

$$\omega'_0 = \omega_0 \cdot (1 + \beta A_0) \quad (11)$$


- For every 20dB reduction in closed-loop gain, the 3dB frequency increases by 1 decade
- This results from a constant gain-bandwidth product, which is an intrinsic property of the open-loop amplifier
- Note that this assumes that the impedances in the feedback network are purely real (i.e. resistors only)
- Let's take a look at the closed-loop frequency response as a function of the feedback factor β

```
[9]: betas = np.logspace(-4, 0, num=5)
w = 2*np.pi*np.logspace(0,9,num=100)
plot_CL_freq(120, 10e6, betas, w)
```


Opamp Closed-Loop Frequency Response

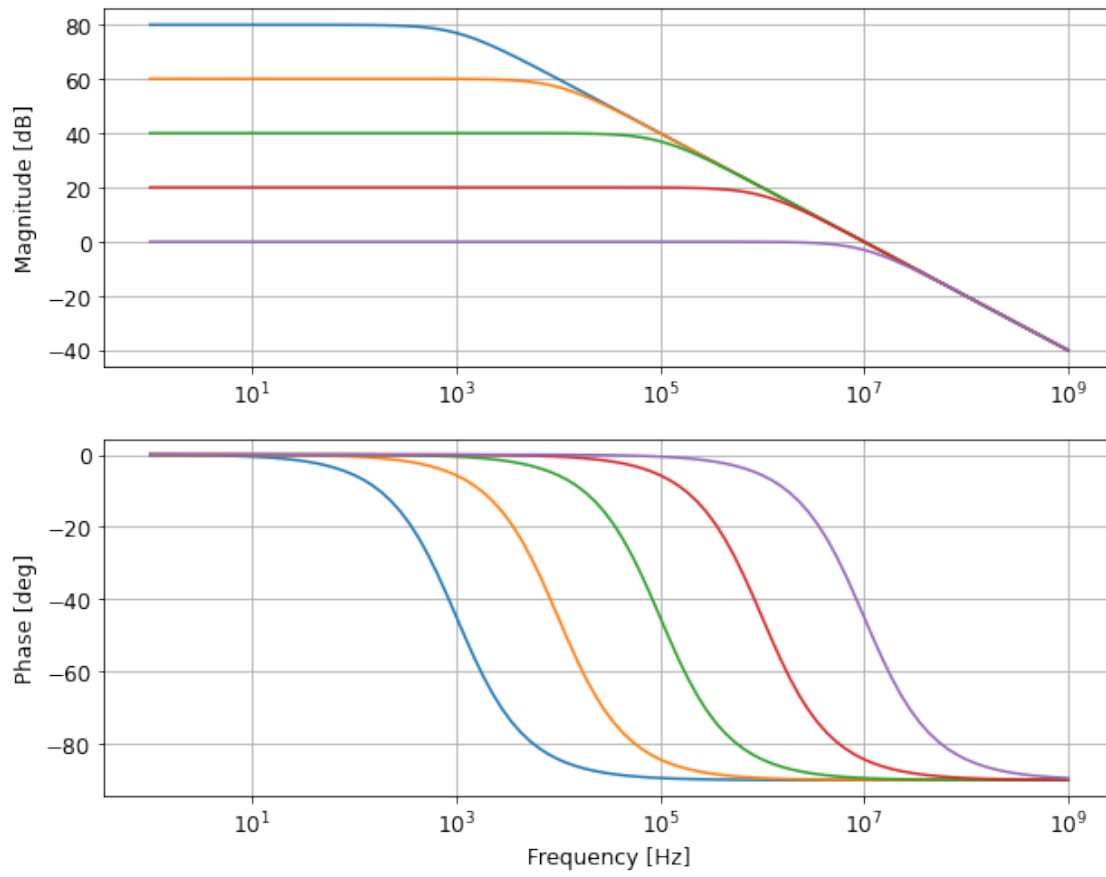

2.8 Stability: Barkhausen criteria

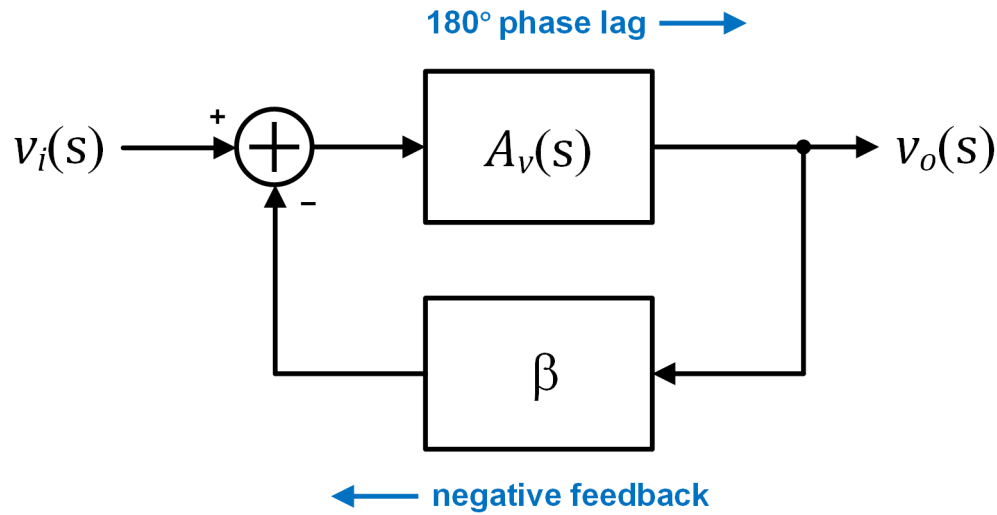

- In a negative feedback loop, if the loop gain at a given frequency ω_1 is -1 , the circuit may oscillate
- This corresponds to a loop gain magnitude $|\beta A_v(j\omega_1)| = 1$ and phase $\angle A_v(j\omega_1) = -180^\circ$

2.9 Stability: Root locus

- Open-loop transfer function

$$A_v(s) = \frac{A_0}{1 + \frac{s}{\omega_0}} \quad (12)$$

- Closed-loop transfer function

$$G(s) = \frac{A_0}{1 + s/\omega_0 + \beta A_0} \quad (13)$$

- Open-loop pole

$$s_0 = -\omega_0 \quad (14)$$


- Closed-loop pole


$$s'_0 = -\omega_0(1 + \beta A_0) \quad (15)$$

- Root locus plots involve plotting the closed-loop poles in the complex plane to evaluate stability
- If a given pole $s = j\omega + \sigma$ falls in the right half plane (RHP), the system is unstable (phase lag $> 180^\circ$)

- Here, for a single pole system, we have a single, real, *LHP* pole, so the system is unconditionally stable

2.10 Bode plot vs root locus

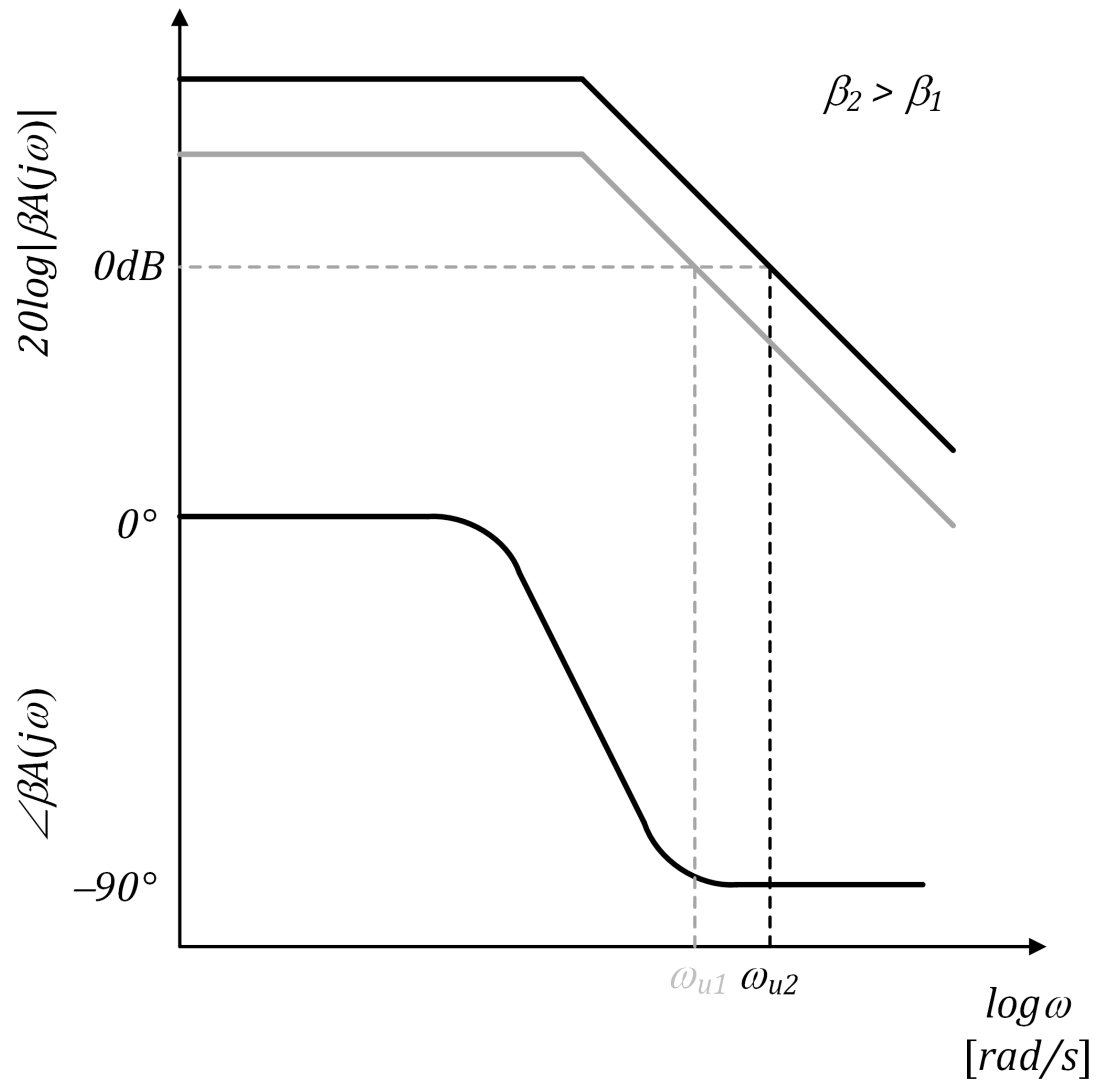

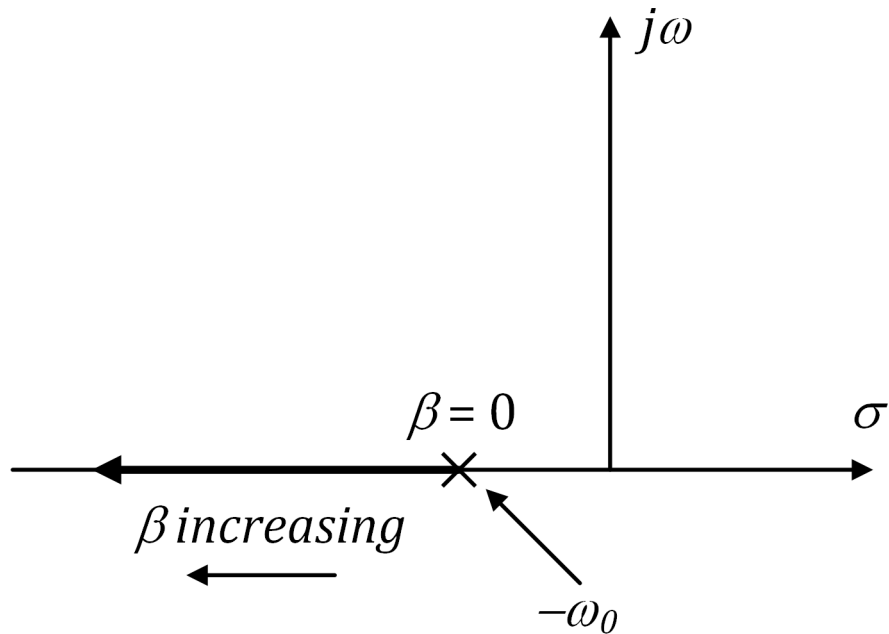

- For a single-pole system both methods indicate unconditional stability:
 - Bode plot: Maximum phase lag of 90°
 - Root locus: Purely real, *LHP* pole
- For higher-order systems, the worst-case scenario arises when $\beta = 1$ (highest possible loop gain)

2.11 Root locus of a second-order system


- Open-loop transfer function

$$A_v(s) = \frac{A_0}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)} \quad (16)$$

- Closed-loop transfer function

$$A_v(s) = \frac{A_0}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) + \beta A_0} \quad (17)$$

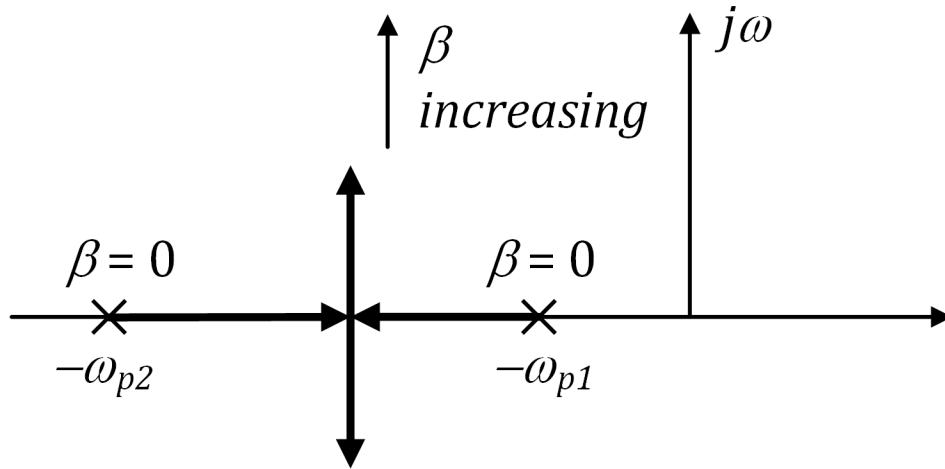- For a second-order system, the situation is more “complex”
- We can solve for the closed-loop pole locations using the quadratic formula and plot them in the complex plane to evaluate stability




- The closed-loop poles are given by

$$s_{p1,2} = \frac{-(\omega_{p1} + \omega_{p2}) \pm \sqrt{(\omega_{p1} + \omega_{p2})^2 - 4(1 + \beta A_0)\omega_{p1}\omega_{p2}}}{2} \quad (18)$$

- When $\beta = 0$ (no feedback), the closed-loop poles are equal to the open-loop poles
- As β increases, the imaginary components of s_{p1} and s_{p2} increase

2.12 Damping ratio and phase margin

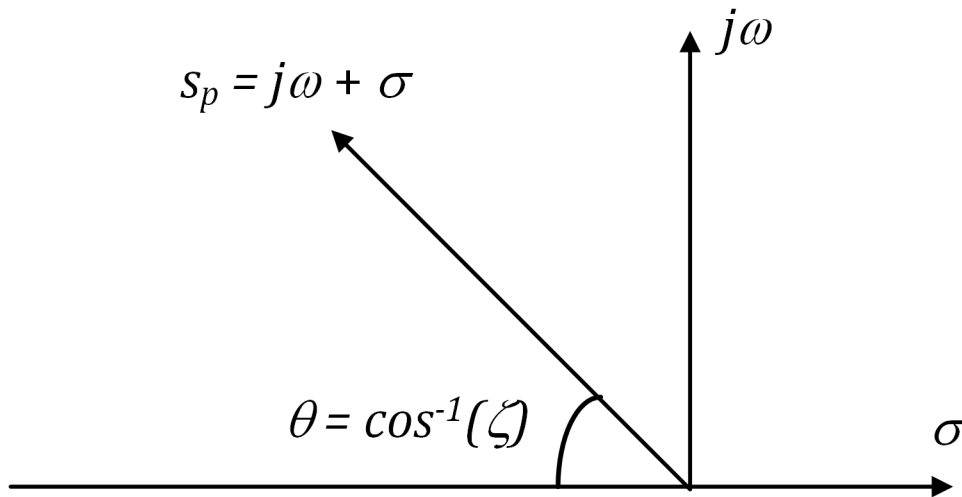


$$PM = \tan^{-1} \frac{2\zeta}{-2\zeta^2 + \sqrt{1 + 4\zeta^2}} \quad (19)$$

- As β increases, the angle $\cos^{-1}(\zeta)$ increases, the magnitude of the imaginary component increases relative to that of the real component
- ζ is referred to as the “damping factor,” and can be used to evaluate the qualitative behavior of the impulse response

- Another means of evaluating this behavior is by looking at the phase margin, which enables use of the Bode plot

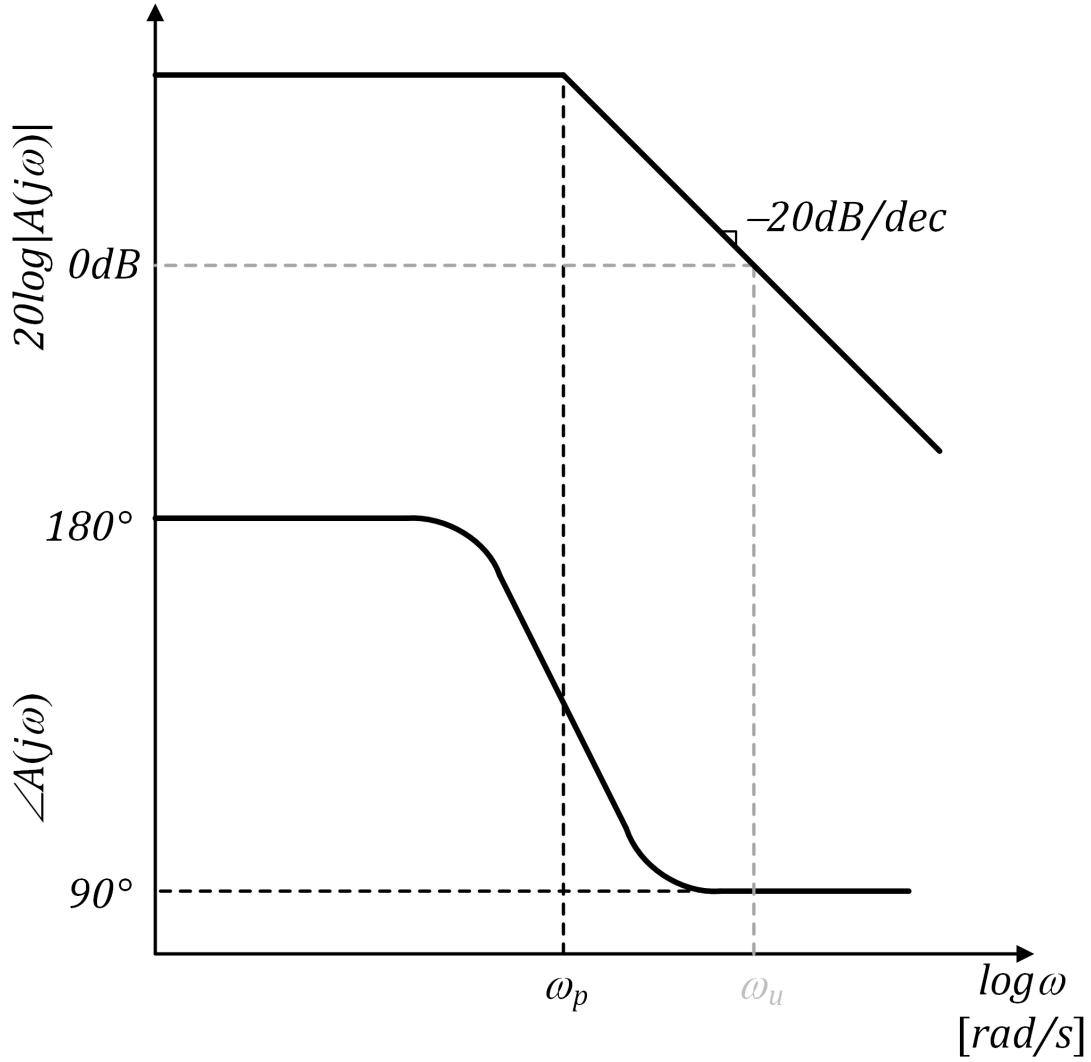2.13 Phase margin of a single-pole system



- Here, phase margin is defined as

$$PM = \angle A(j\omega_u) - 0^\circ \quad (20)$$

- For a single-pole system, the phase margin is


$$PM = \angle A(j\omega_u) = 180^\circ - \tan^{-1} \frac{\omega_u}{\omega_{p1}} \quad (21)$$

- This has a minimum value of

$$PM \geq 180^\circ - 90^\circ = 90^\circ \quad (22)$$

- This guarantees stability and a “well behaved” step response

2.14 Phase margin of a two-pole system

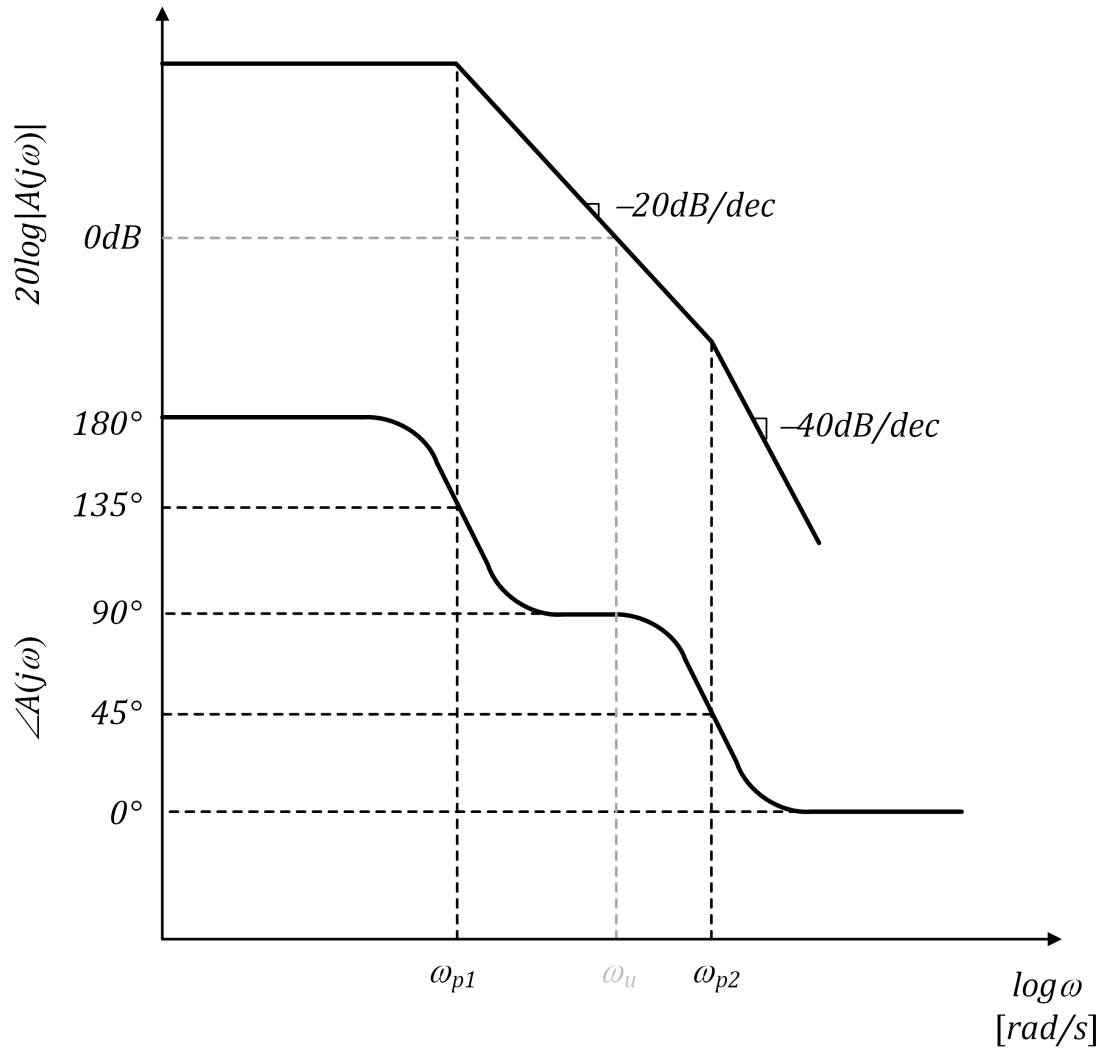

- For stability (i.e. no oscillation), we need

$$\angle A(j\omega_u) > 0^\circ \quad (23)$$

- For a well-behaved response, we prefer to have

$$\angle A(j\omega_u) \geq 60^\circ \quad (24)$$


- This places a requirement on ω_{p2} of

$$\tan^{-1} \frac{\omega_u}{\omega_{p2}} \leq 30^\circ \quad (25)$$

$$\omega_{p2} \geq 1.73\omega_u$$


(26)

2.15 Telescopic cascode amplifier

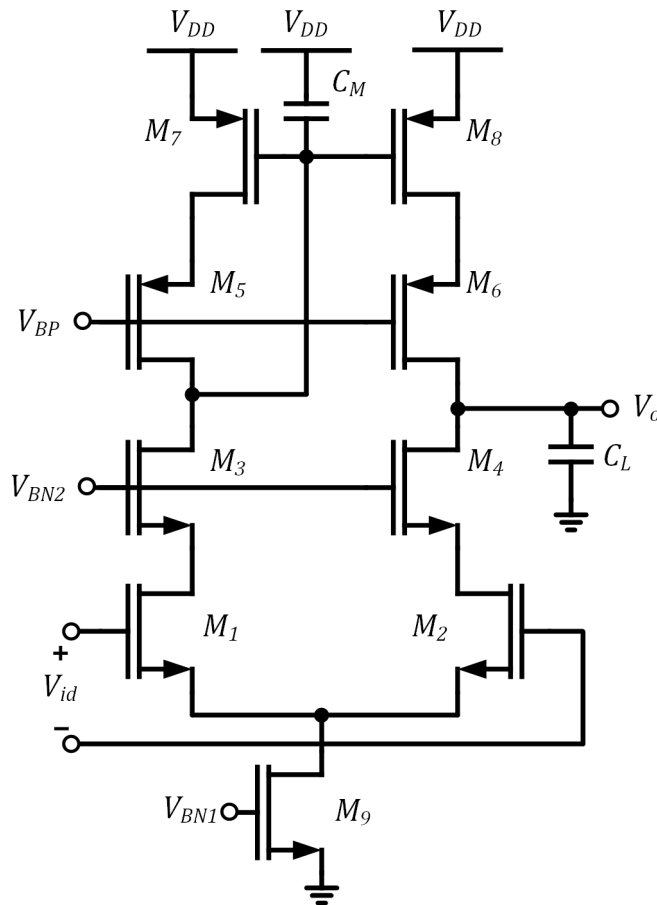

- C_M represents parasitic capacitance at the gate node of M_7, M_8
- C_M may be large if $V_{OV7,8}$ is small
- M_7 gate connection functions as a diode-connected MOS in the small-signal model
- The $3dB$ frequency can be found by ZVTC analysis, but assuming $C_L \gg C_M$, it can be approximated as the product of R_o and C_L

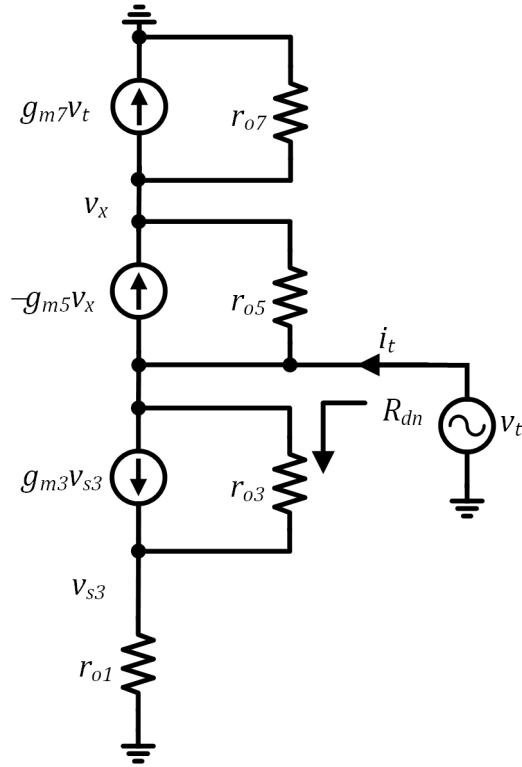2.16 M7 diode connection (small signal analysis)



$$i_{up} = \frac{v_t - v_x}{r_{o5}} - g_{m5}v_x \quad v_x = \frac{v_t - i_{up}r_{o5}}{g_{m5}r_{o5} + 1} \quad (27)$$


$$i_{up} = g_{m7}v_t + \frac{v_x}{r_{o7}} = g_{m7}v_t + \frac{v_t - i_{up}r_{o5}}{r_{o7}(g_{m5}r_{o5} + 1)} \quad (28)$$

$$i_{up} \left(1 + \frac{r_{o5}}{r_{o7}(g_{m5}r_{o5} + 1)} \right) = v_t \left(g_{m7} + \frac{1}{r_{o7}(g_{m5}r_{o5} + 1)} \right) \quad (29)$$

- The output resistance is thus

$$R_{up} = \frac{v_t}{i_{up}} \approx \frac{1}{g_{m7}} \quad (30)$$

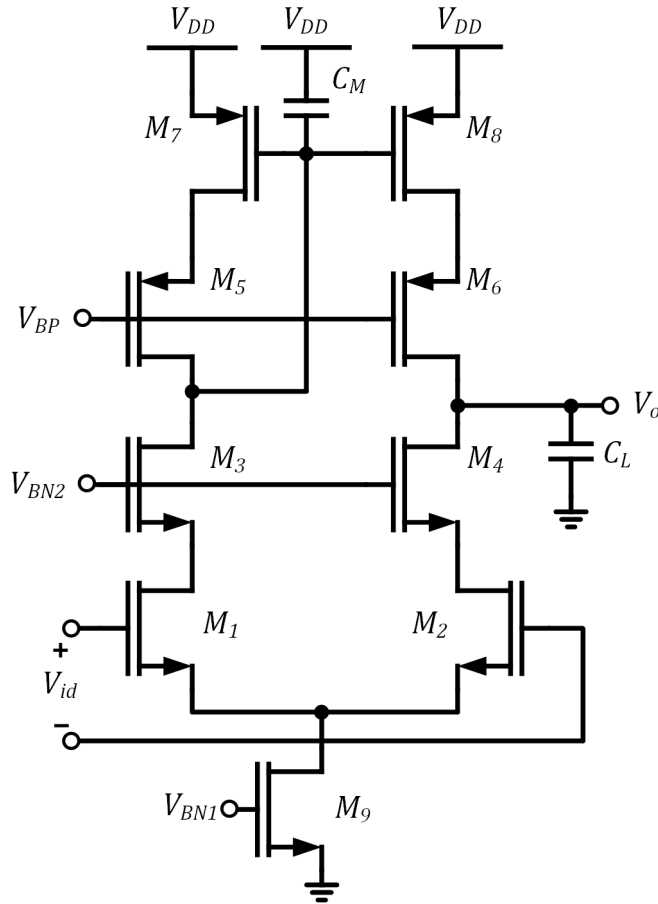2.17 Telescopic amplifier frequency response



- The dominant pole frequency is

$$\omega_{p1} \approx \frac{1}{g_{m6}r_{o6}r_{o8}||g_{m4}r_{o4}r_{o2}} \quad (31)$$

- The non-dominant pole is given by

$$\omega_{p2} \approx \frac{g_{m7}}{C_M} \quad (32)$$


- Assuming $\omega_{p2} \gg \omega_{p1}$, the gain-bandwidth is

$$\omega_u \approx \frac{g_{m1,2}}{C_L} \quad (33)$$

- The phase is

$$\angle A(j\omega) = 180^\circ - \tan^{-1} \frac{\omega}{\omega_{p1}} - \tan^{-1} \frac{\omega}{\omega_{p2}} \quad (34)$$

2.18 Telescopic amplifier phase margin

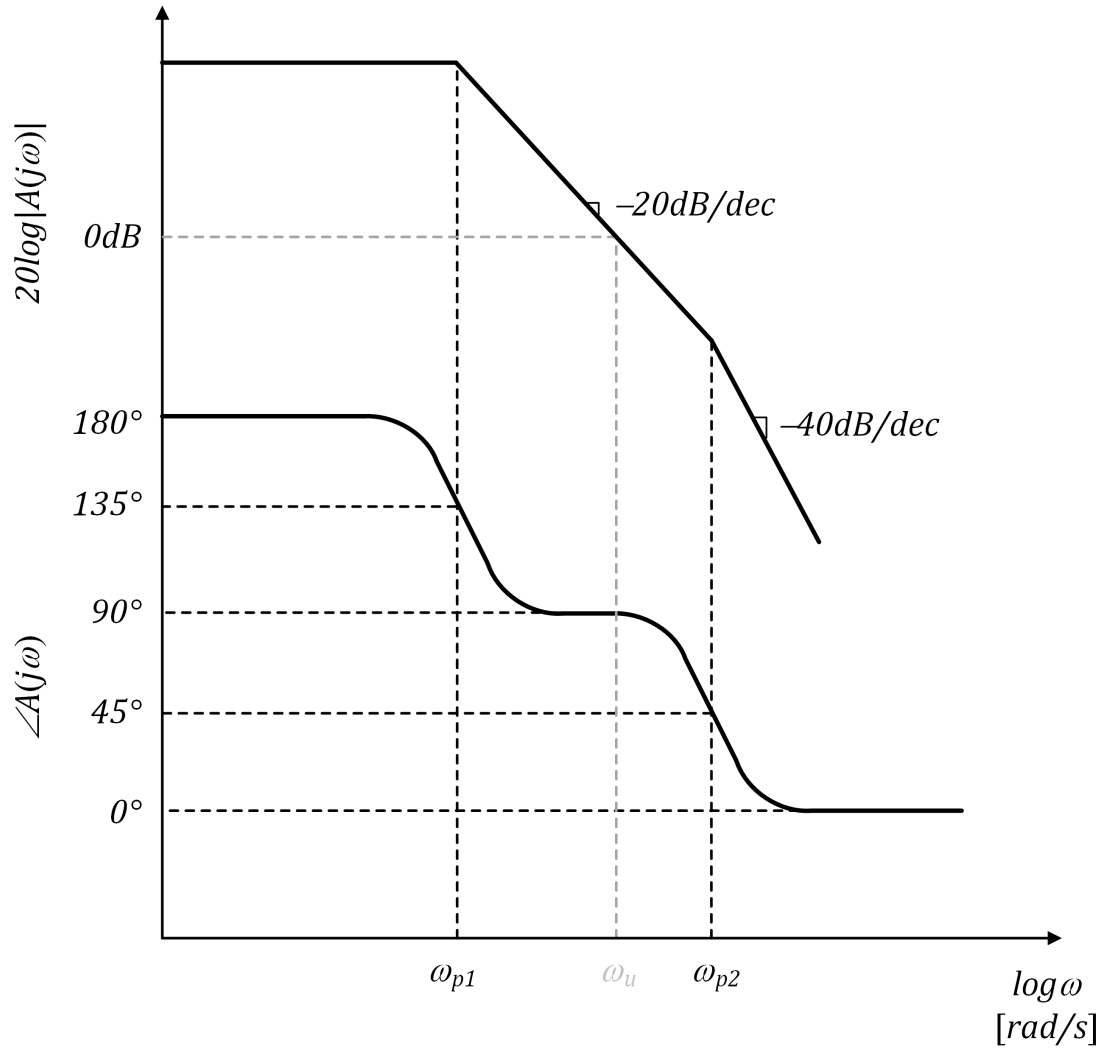

- For a well-behaved response we need


$$A(j\omega_u) \geq 60^\circ \quad (35)$$

- Assuming a two-pole amplifier, this requires

$$\frac{g_{m7}}{C_M} \geq 1.73 \frac{g_{m1,2}}{C_L} \quad (36)$$

- If constant bandwidth ($g_{m1,2}/C_L$) is assumed, either g_{m7} or C_M needs to be minimized to meet this requirement
- Both terms can be reduced by reducing $W_{7,8}$ while keeping L constant (this will increase $V_{OV7,8}$)

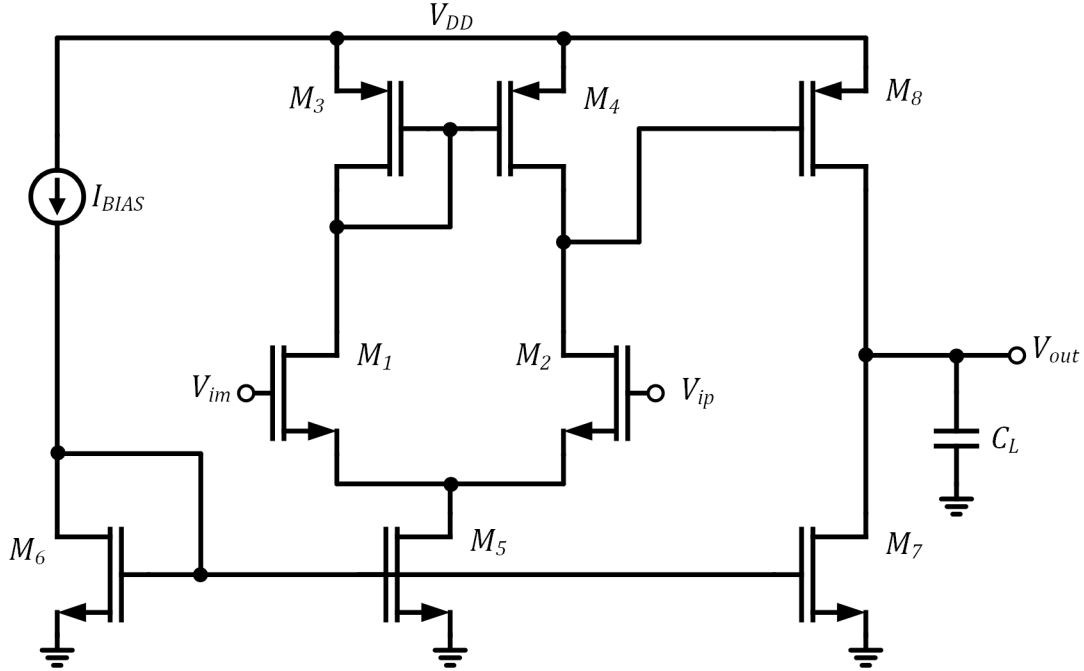2.19 Frequency response of a 2-stage amplifier



- A 2-stage amplifier can be analyzed in the same manner as a common-source amplifier
- Here we primarily focus on the second stage, due to the high output impedance of the first stage ($R_{o1} = r_{o2} || r_{o4}$) and the Miller effect of M_8
- The DC gain of the amplifier is given by the product of the gains of the individual stages:

$$A_0 = G_{m1} R_{o1} G_{m2} R_{o2} \quad (37)$$

$$= g_{m1} r_{o2} || r_{o4} \cdot g_{m8} r_{o8} || r_{o7} \quad (38)$$

- Let's take a look at the frequency response...
- Assuming the mirror pole is well above the unity-gain bandwidth of the amplifier, the 2-stage CMOS OTA can be analyzed as a common-source amplifier with $R_{o1} = r_{o2} || r_{o4}$ as the output impedance of the driving stage
- In this case, the transfer function is given as

$$A_v(s) = g_{m1} R_{o1} \frac{(sC_{GD} - g_{m8})R_{o2}}{R_{o1}R_{o2}\zeta s^2 + [R_{o1}(1 + g_{m8}R_{o2})C_{GD} + R_{o1}C_{GS} + R_{o2}(C_{GD} + C_L)]s + 1} \quad (39)$$

$$(40)$$

- If we allow $R_{o2} \rightarrow \infty$ (this places the dominant pole at the origin), this becomes

$$\lim_{R_{o2} \rightarrow \infty} A_v(s) \approx g_{m1} R_{o1} \frac{(sC_{GD} - g_{m8})}{s[R_{o1}(C_{GS}C_{GD} + C_{GS}C_L + C_{GD}C_L)s + g_{m8}R_{o1}C_{GD} + (C_{GD} + C_L)]} \quad (41)$$

$$(42)$$

- The assumption that $R_{o2} \rightarrow \infty$ is equivalent to the second stage being a “perfect integrator” (i.e. infinite gain).
- We can solve for the non-dominant pole by setting the denominator equal to zero and solving for s . This gives

$$\omega_{p2} \approx \frac{(g_{m8}R_{o1} + 1)C_{GD} + C_L}{R_{o1}(C_{GS}C_{GD} + C_{GS}C_L + C_{GD}C_L)} \quad (43)$$

- This can be further approximated by assuming $g_m R_{o1} C_{GD} \gg C_L$

$$\omega_{p2} \approx \frac{g_{m8}R_{o1}C_{GD}}{R_{o1}(C_{GD}(C_{GS} + C_L) + C_{GS}C_L)} \quad (44)$$

- We have previously shown the dominant pole of the transfer function to be well-approximated as

$$\omega_{p1} \approx \frac{1}{R_{o1}(1 + g_{m8}R_{o2})C_{GD}} \quad (45)$$

2.20 Pole splitting

- With the two poles of the transfer function given by

$$\omega_{p1} \approx \frac{1}{R_{o1}(1 + g_{m8}R_{o2})C_{GD}} \quad \omega_{p2} \approx \frac{g_{m8}C_{GD}}{C_{GD}(C_{GS} + C_L) + C_{GS}C_L} \quad (46)$$

- We can make some qualitative observations about their behavior:
 - As C_{GD} increases, ω_{p1} decreases, lowering bandwidth
 - ω_{p2} simultaneously increases as the C_{GD} term in the denominator becomes dominant
 - ω_{p2} is ultimately limited by $g_{m8}/(C_{GS} + C_L) \approx g_{m8}/C_L$
- This behavior is referred to as “pole splitting,” since ω_{p1} and ω_{p2} are moving in opposite directions as C_{GD} is increased

2.21 2-stage amplifier RHP zero

- The full transfer function is once again given by

$$A_v(s) = \frac{(sC_{GD} - g_{m8})R_{o2}}{R_{o1}R_{o2}\xi s^2 + [R_{o1}(1 + g_{m8}R_{o2})C_{GD} + R_{o1}C_{GS} + R_{o2}(C_{GD} + C_L)]s + 1} \quad (47)$$

$$(48)$$

- The expression in the numerator, $N(j\omega) = (sC_{GD} - g_{m8})R_{o2}$ results in a zero in the right half of the complex plane

$$\omega_z = \frac{g_{m8}}{C_{GD}} \quad (49)$$

- A zero in the right-half plane increases phase lag as well as gain magnitude, which can be detrimental to stability

$$\angle N(j\omega) = \tan^{-1} \left(-\frac{\omega C_{GD}}{g_{m8}} \right) \quad (50)$$

2.22 Phase margin

- If we assume dominant-pole behavior, we can approximate the unity-gain frequency as

$$\omega_u \approx g_{m1}R_{o1}g_{m8}R_{o2} \cdot \frac{1}{g_{m8}R_{o2}R_{o1}C_{GD}} = \frac{g_{m1}}{C_{GD}} \quad (51)$$

- The phase margin can then be approximated as

$$PM \approx 90^\circ - \tan^{-1} \frac{\omega_u}{\omega_{p2}} - \tan^{-1} \frac{\omega_u}{\omega_z} \quad (52)$$

$$= \boxed{90^\circ - \tan^{-1} \frac{g_{m1}C_L}{g_{m8}C_{GD}} - \tan^{-1} \frac{g_{m1}}{g_{m8}}} \quad (53)$$


$$(54)$$

- Note that if g_{m1} and g_{m8} are comparable, and if $C_L \geq C_{GD}$, the phase margin will be zero, or even negative!

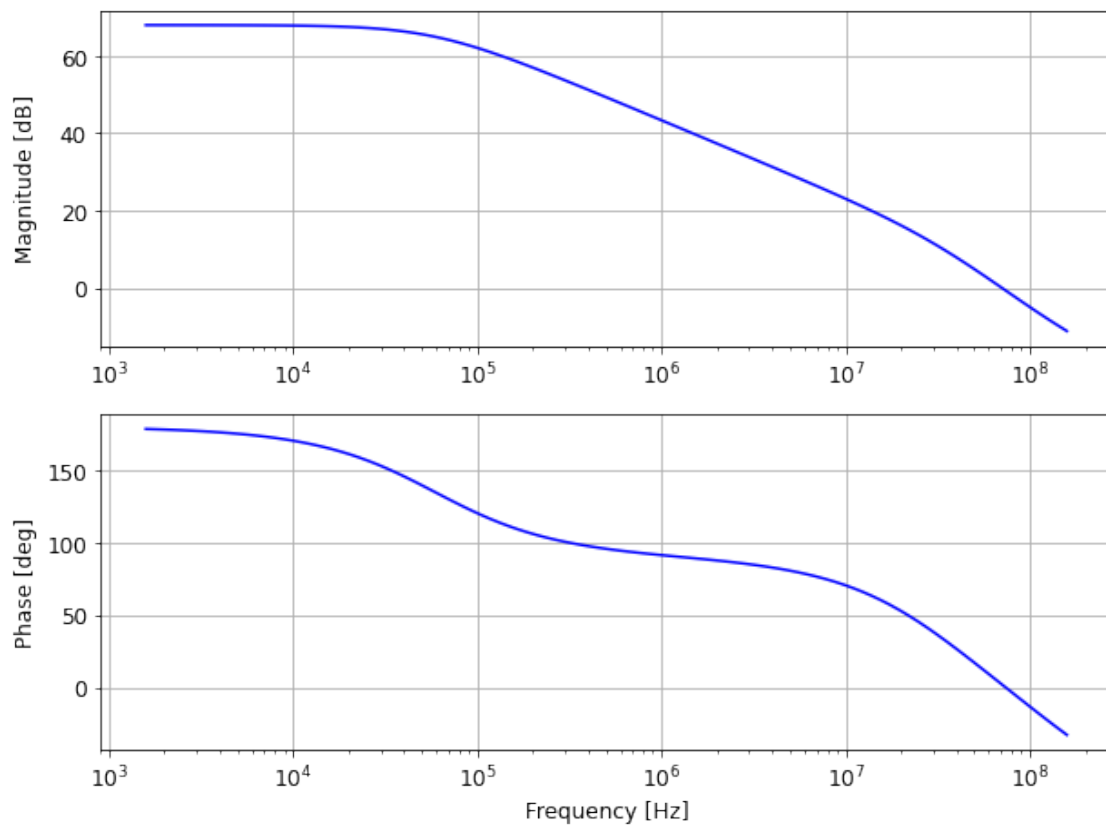2.23 Frequency response

```
[222] : gm1 = 1e-3
gm8 = 1e-3
ro = 100e3
R_o1 = ro/2
R_o2 = ro/2
C_GD = 1e-12
C_GS = 2e-12
C_L = 1e-12
zeta = C_GS*C_GD + C_GS*C_L+C_GD*C_L
num = [C_GD*R_o2*gm1*R_o1, -gm8*R_o2*gm1*R_o1]
den = [R_o1*R_o2*zeta, gm1*R_o1*R_o2*C_GD+R_o1*C_GS+R_o2*(C_GD+C_L), 1]
tf_CS = signal.TransferFunction(num, den)
w, mag, phase = tf_CS.bode()
f = w/2/np.pi
```

```
[223]: plot_logxy2(f, mag, f, phase, 'Frequency [Hz]', 'Magnitude [dB]',
                  'Frequency [Hz]', 'Phase [deg]')
```



2.24 Summary

- The frequency response of closed-loop amplifiers relies on characteristics of the open-loop response
- Stability of negative-feedback systems requires a phase lag of less than 180° at the transit (unity-gain) frequency
- Bode plots and root loci can be used to evaluate stability of closed-loop systems
- To ensure “well-behaved” closed-loop responses, phase margin should be kept above $\sim 60^\circ$ (critical damping, no overshoot)
- Mirror pole can degrade phase margin in single-ended OTAs
- 2-stage OTAs have multiple poles and a RHP zero
- Next time, we’ll look at compensation of 2-stage CMOS OTAs